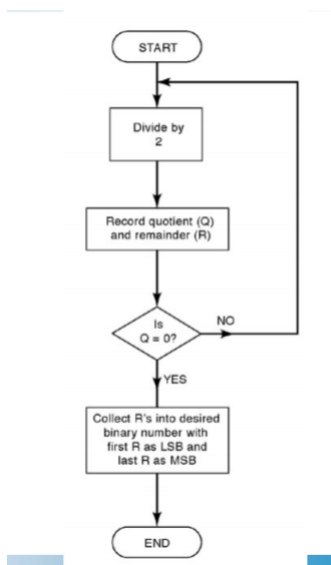


DIGITAL SYSTEM

1 Digital and Analog Systems

- **Digital System** is a combination of devices that manipulate values represented in digital form.
- **Analog System** is a combination of devices that manipulate values represented in analog form.

Analog-to-digital conversion(ADC) and digital-to-analog conversion(DAC) complicate circuitry



2 Digital Number Systems

- Number system differ in the number of symbols they use

- Decimal - 10 symbols (base 10)
- Hexadecimal - 16 symbols (base 16)
- Octal - 8 symbols (base 8)
- Binary - 2 symbols (base 2)

3 Conversion

Binary to Decimal Conversion

1 0 0 1 0 1₂

5 4 3 2 1 0 We consider that:

$$(100101)_2 = 1 \times 2^5 + 0 \times 2^4 + 0 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 = (37)_{10}$$

Decimal to Binary Conversion


$$\frac{41}{2} = 20 \quad a_0 = 1 \quad \frac{5}{2} = 2 \quad a_3 = 1$$

$$\frac{20}{2} = 10 \quad a_1 = 0 \quad \frac{2}{2} = 1 \quad a_4 = 0$$

$$\frac{10}{2} = 5 \quad a_2 = 0 \quad \frac{1}{2} = 0 \quad a_5 = 1$$

$$(41)_{10} = (a_5 a_4 a_3 a_2 a_1 a_0)_2 = (101001)_2$$

Flow chart:

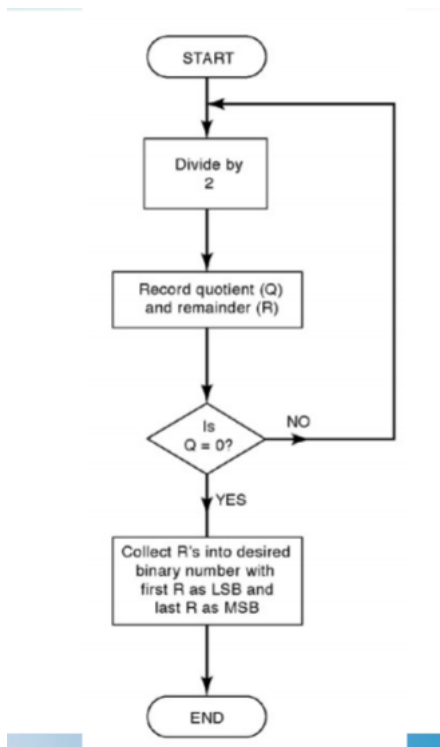

Convert from Hexadecimal to Decimal

- Convert from Hexadecimal to decimal by multiplying each hex digit by its positional weight

$$\begin{aligned} 163_{16} &= 1 \times (16^2) + 6 \times (16^1) + 3 \times (16^0) \\ &= 1 \times 256 + 6 \times 16 + 3 \times 1 \\ &= 355_{10} \end{aligned}$$

Hexadecimal to Decimal Conversion

- Convert from Hexadecimal to Decimal by dividing the decimal number by 16
- Same method to conversion from binary to decimal

Hexadecimal to Binary Conversion

$$\begin{aligned} 9F2_{16} &= 9 \quad F \quad 2 \\ &1001 \quad 1111 \quad 0010 = \\ &100111110010_2 \end{aligned}$$

Binary to Hexadecimal Conversion

- To convert Binary to Hexadecimal, first we should group bits in four, then we convert each group to hexadecimal.
- Ex:
- $$\begin{aligned} 1110100110_2 &= 0011 \ 1010 \ 0110 \\ &= 3 \ A \ 6 \\ &= 3A6_{16} \end{aligned}$$

4 BCD

- **Binary Coded Decimal (BCD)** is another way to present decimal numbers in binary form.

- BCD is widely uses and combines features of both decimal and binary systems.
- Each digit is converted to a binary equivalent.

Bảng 1: BCD Table

Decimal	BCD
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001

- To convert the number 874_{10} to BCD:

$$\begin{array}{ccc} 8 & 7 & 4 \\ 1000 & 0111 & 0100 \end{array} = 100001110100_{\text{BCD}}$$

- Each decimal digit is represented using 4 bits
- Each 4-bit group can never be greater than 9.
- Reverse the process to convert BCD to decimal.

5 Flip Flop

- So far we has seen Combinational Logic that the output(s) depends only on the value of the input variables.
- Here we look at Sequential Logic circuit that the output(s) can depend on


present and also past values of the input and output variables.

- Sequential circuits exist only in one of a defined number of state at any one time.

5.1 Synchronous and Asynchronous Sequence Logic:

- Synchronous:
 - The timing of all state transitions is controlled by a common clock.
 - Changes in all variables occur simultaneously.
- Asynchronous:
 - State transitions occur independently of any clock and normally dependent on the timing of transitions in the input variables.
 - Changes in more than one output do not necessarily occur simultaneously.
- Clock:
 - A clock signal is a square wave of fixed frequency.
 - Often, transitions will occur on one of the clock pulses

 5.2 General Flip Flop Symbol and definition of its two possible output states



- The Flip Flop, abbreviated FF, is a key memory element.
- The output of the Flip Flop is Q and \bar{Q} .
- Q is understood to be the normal output, \bar{Q} is always the opposite.
- The most basic circuit can be constructed from either two NAND gates or NOR gates.

5.3 NAND gate latch

- The inputs are **set** and **clear** (reset).
- The inputs are active low, that is, the output will change when the input is pulsed low.
- When the latch is set:

$$Q = 1 \text{ and } \bar{Q} = 0$$

- When the latch is clear or reset:

$$Q = 0 \text{ and } \bar{Q} = 1$$

Summary of NAND latch

- SET = RESET = 1: Normal resting state, outputs remain in state prior to output.
- SET = 0, RESET = 1: Q will go high and remain high even if the SET input goes high.
- SET = 1, RESET = 0: Q will go low and remain low even if the SET input goes high.
- SET = RESET = 0: Output is unpredictable because the latch is being set and reset at the same time.


5.4 NOR Gate Latch

- The NOR Gate Latch is similar to the NAND Gate Latch, except that the output Q and \bar{Q} is reserved.
- **The inputs are active high**, that is, the outputs will change only the inputs **are pulsed high**.
- In order to ensure that a FF begins operation at a known level, a pulse may be applied to SET and RESET inputs when a device is powered up.

5.5 Digital Pulses

- In digital system, when a signal switches from a normal inactive state to the opposite (active) state, thus causing something happen in the circuit. Then the signal returns to its inactive state while the effect of the recently activated signal remains in the system. These signals are called pulses.

FIGURE 5-14 (a) A positive pulse and (b) a negative pulse.

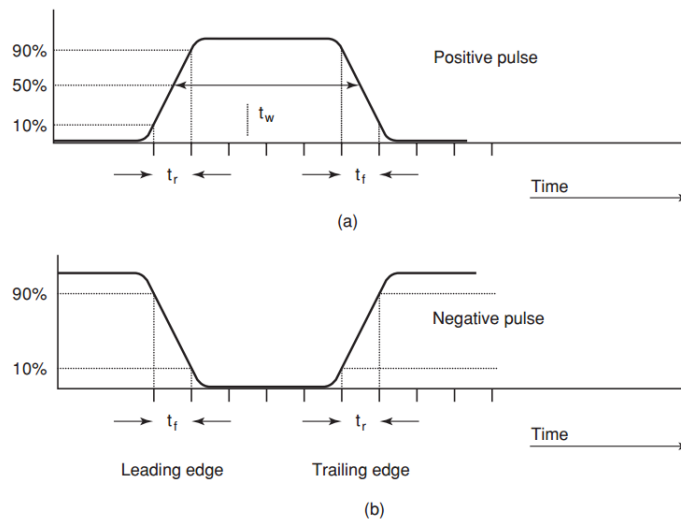

- A pulse that performs its intended function when it goes HIGH is called a positive pulse.
- A pulse that performs its intended function when it goes LOW is called a negative pulse.
- The transition from low to high on a positive pulse is called rise time (t_r).
- The transition from high to low on a positive pulse is called fall time (t_f).
- The transition from the beginning of the pulse is called the leading edge and the transition at the end of the pulse is called the trailing edge.


5.6 Clock Signal and CLocked Flip Flop

- Digital system can be operate either asynchronously and synchronously:

- In asynchronous system, the outputs of circuits can change state any-time one or more of the inputs change.
- In synchronous system, the outputs can change states at the exact time by a signal called clock. This clock signal is generally a rectangular pulse train or a square wave.

Clock Signal

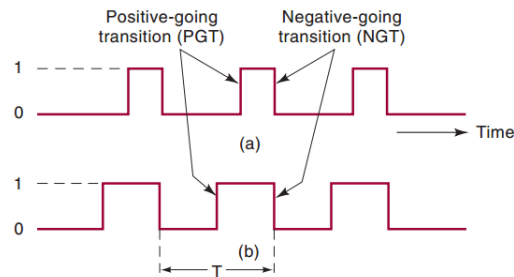- Most (if not all) of the system outputs can change state only when the clock make a transition.



- A transition (also called *edges*):

- When the clock changes from 0 to 1, this is called the **positive-going transition (PGT)**.
- When the clock changes from 1 to 0, this called the **negative-going transition (NGT)**.

- Most digital system are principally synchronous (although there are always some asynchronous parts) because synchronous circuits are easier to design and troubleshoot.

Clocked Flip Flop

- Clocked FFs can change state on one or other clock transitions. Some common characteristics:
 - Clock inputs are labeled as CLK, CK, or CP.
 - A **small triangle** at the CLK input indicates that CLK input is

activated with a PGT (positive-going transition).


- A **bubble and a triangle** at the CLK input indicates that CLK input is activated with a NGT (negative-going transition).
- Control inputs have an effect on the output only at the active clock transition (PGT and NGT). There are also called synchronous control inputs.
- The control inputs get the FF outputs ready to change, but the change is not triggered until the CLK edge.

Setup Time and Hold Time

- Setup time (t_s) is the minimum time interval before the active CLK transition that the control input must be kept at the proper level.
- Hold time (t_h) is the time after the active CLK transition during which the control input must be kept at the proper level.

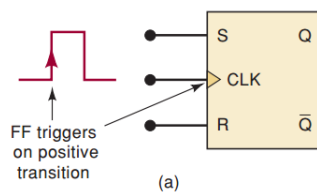5.7 Clocked S-R Flip Flop

- In Clocked S-R Flip Flop system, FF only change states when when a signal applied to its clock input makes a transition from 0 to 1 or from 1 to 0 (PGT and NGT).
- The up arrow (\uparrow) indicates that a PGT is required at CLK; the label Q_0 indicates the level at Q prior to the PGT.




Inputs			Output
S	R	CLK	Q
0	0	\uparrow	Q_0 (no change)
1	0	\uparrow	1
0	1	\uparrow	0
1	1	\uparrow	Ambiguous

Q_0 is output level prior to \uparrow of CLK.
 \downarrow of CLK produces no change in Q.

(b)

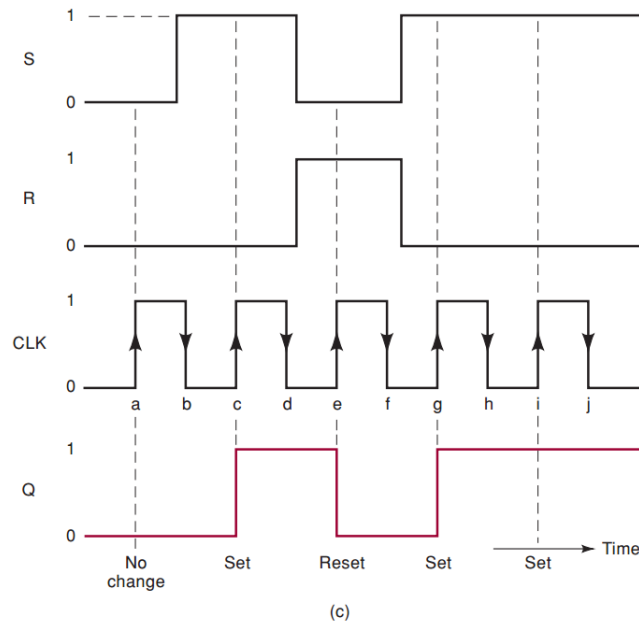- We can analyze these waveforms as follows:




1. Initially all inputs are 0 and the Q output is assumed to be 0; that is $Q_0 = 0$
2. When the PGT of the first clock pulse occurs (point a), the S and R inputs are both 0, so the FF is not effected and remains in the $Q = Q_0$ state ($Q = Q_0$)
3. When the PGT of the second clock pulse (point c), the $S = 1$ and $R = 0$. Thus the FF set to 1 state at the rising edge of this clock pulse.
4. When the third clock pulse makes its positive transition (point e) $S = 0$ and $R = 1$. Thus it causes the FF set to 0 state.
5. At the fourth pulse set the FF once again to the $Q = 1$ state (point g) because $S = 1$ and $R = 0$ when PGT occurs
6. The fifth pulse also find that $S = 1$ and $R = 0$ at PGT occurs so the FF remains state.
7. The case that $S = R = 1$ should not be used because it results in an ambiguous condition.

8. It should be noted that those waveforms that the FF is **not effected** by the NGT of the clock pulses. Also note that the S and R levels have no effects on the FF, except upon the occurence of the PGT **in PGT transitions**
 9. For the NGT transition the FF operate at the same manner at PGT transition, except the output can change states only on the falling edge of the clock pulse
- As a general rule for stable flip flop triggering, the clock pulse rise and fall time must be very short, around typically 2 - 5 ns.

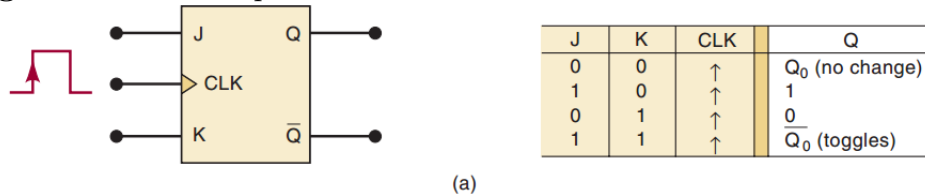5.8 Clocked J-K Flip Flop


- The J and K inputs control the state of the FF in the same way as the S and R inputs do for the clocked S-R flip flop, except 1 difference that when $J = K = 1$ condition **does not result** in ambiguous output. In this condition, the FF will always go to its opposite side of the clock signal, this is called **toggle mode** of the operation.



- The operation of the J-K Clocked Flip Flop is the same as the S-R Clocked Flip Flop, except when $J = K = 1$ at the PGT transition the output will change to the opposite state.
- Also in NGT, the operation is still same as PGT when clock is triggered in NGT.
- In edge-triggered J-K Flip Flop, CLK^* must be high for FF to change states. This condition only occurs at the edge of a CLK transition

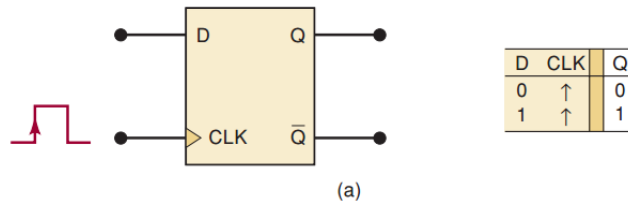5.9 Clocked D Flip Flop


- Unlike the S-R and J-K Clocked Flip Flop, this flip flop has only one synchronous control input, D , which stands for data.
- The operation of the D Clocked Flip Flop is very simple: Q will go as the same state on the D input when a PGT occurs at CLK.
- A negative-edge-triggered D flip flop operates in the same way and Q will take on the value of D when a NGT occurs at CLK.



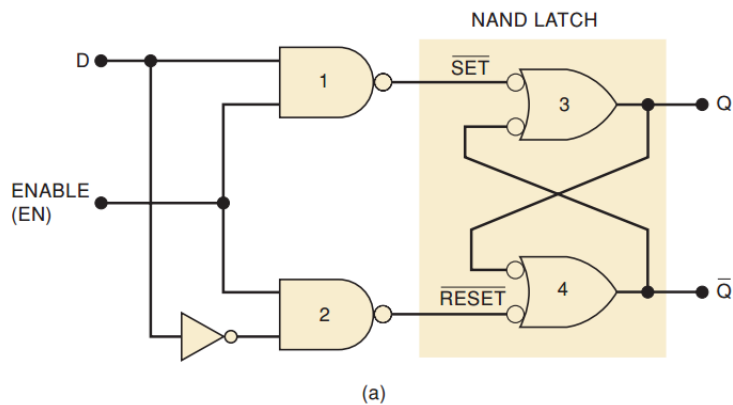5.10 D Latch (Transparent Latch)

- The edge triggered D Flip Flop uses an edge-detector circuit to ensure that the output will respond to the D input only when the active transition of the clock occurs. The latch that its edge-detector is not used called the D latch.

- One data input.
- The clock has been replaced by an ENABLE (EN).
- The device is not edge-triggered.
- When $EN = 1$; the output follows the change of input.
- When $EN = 0$; whether D changes or not Q will stay at their current level (no change).




Inputs		Output
EN	D	Q
0	X	Q_0 (no change)
1	0	0
1	1	1

X indicates "don't care."
 Q_0 is state Q just prior to EN going LOW.


(b)

- Logic symbol of D latch:

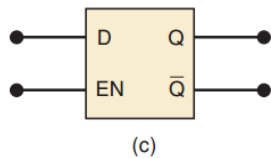

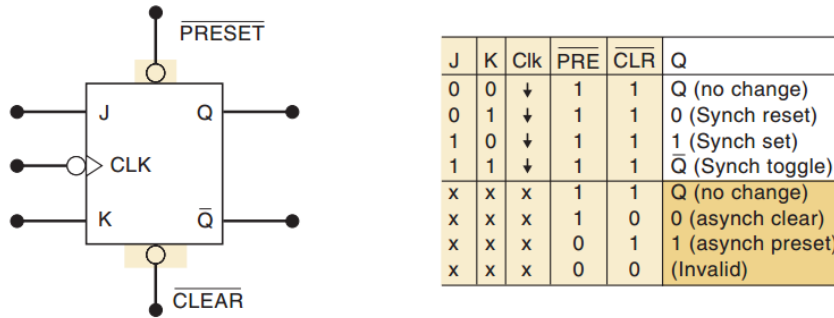5.11 Asynchronous Inputs

- For the clocked flip flop, the S-R, J-K and D inputs have been referred as **synchronous inputs**
- Most clocked FF also have one or more asynchronous inputs that operate independently of the synchronous inputs.
- These asynchronous inputs can be used to set FF to the 1 state of clear (reset) and FF to 0 state at **any time, regardless conditions of inputs**.
- State in another way, the asynchronous inputs are **override inputs**



- $\overline{PRESET} = \overline{CLEAR} = 1$: The asynchronous inputs are inactive and the output depend only on CLK transitions.
- $\overline{PRESET} = 0; \overline{CLEAR} = 1$: The \overline{PRESET} is activated and $Q = 1$ (no matter what conditions). The CLK inputs cannot affect the FF while $\overline{PRESET} = 0$.
- $\overline{PRESET} = 1; \overline{CLEAR} = 0$: The \overline{CLEAR} is activated and $Q = 0$ (no matter what conditions). The CLK inputs cannot affect the FF while $\overline{CLEAR} = 0$.
- $\overline{PRESET} = \overline{CLEAR} = 0$: Ambiguous response.

6 Flip Flop Timing Consideration

6.1 Setup and Hold Times

- Setup time and Hold time represent for reliable FF triggering. In IC's datasheet will always spectify the minimum values of t_s and t_h

6.2 Propagation Delays

- Whenever a signal is to change the state of a FF's output, there is delay from the time the signal is applied to the time when the output makes its

change.

- The delay is measured between 50 percent points on the input and output waveform.
- Modern IC flip-flops have propagation delay that ranges from a few ns to 100 ns.

6.3 Maximum Clocking Frequency (f_{Max})

- This is the highest frequency that may be applied to the CLK input of a FF and still have it trigger reliably.

6.4 CLock Pusle HIGH and LOW time

- Clock Pulse HIGH is the time when the CLK is kept at HIGH before goes LOW.
- CLock Pulse LOW is the time when the CLK is kept at LOW before goes HIGH.

6.5 Asynchronous active pulse width

- The minimum time that PRESET or CLEAR must be held for the FF to set or clear reliably.

6.6 Clock Transition Time

- For reliable triggering, the clock waveform transition times (rise and fall time) should be kept be very short. If the clock signal takes too long to make the transition from 1 level to another, the FF will trigger eratically.
- The transition time should be ≤ 50 ns for TTL devices and ≤ 200 ns for CMOS

7 Potential Timing Problem in FF circuit

- When the output of one FF is connected to the input of another FF and both devices are triggered by the same clock, there is a potential timing problem.
- Propagation time delay may cause unpredictable outputs.
- The problem can be reduced due to low hold time.

8 Flip Flop Synchronization

- Most system are primarily synchronous in their operation most of the signals will change states in synchronism with the clock transition.
- The randomness by asynchronous can produce unpredictable result.

9 Data Storage and Transfer

- Most common of the flip flop is for storage and information.
- The data is stored in groups is called **register**.

10 Fuzzy Logic

- Fuzzy Logic (FL) is a method of reasoning that resemble the human reasoning.
- Unlike Combinational Logic which only takes precise input and produce a definite output as 0 and 1.
- Fuzzy Logic provide the wide range of the output that surround the value of 0 and 1.

- To symplify the the result is 1, we can give the output of around 0.75 or 0.9 when the result is 0, the output can be a 0.34 or 0.2.
- The Fuzzy Logic works on the levels of possiblities of inputs to achieve the definite output.
- Fuzzy LOgic is useful for commercial and practical product.
 - It can control machines and consumer products.
 - It may not give a accurate result, but it still a acceptable result.
 - Fuzzy logic help to deal with the uncertainly in engineering.


10.1 Fuzzy logic system

- It has 4 main parts:

- Fuzzification Module:
 - It transforms the system inputs, from crisp number to fuzzy set.
 - Crisp number is a single point, ex: 3, 5.5, 6; when fuzzy number is a fuzzy set with different degree os closeness to a given crisp number.
 - It splits the input signal into 5 components:

LP	x is Large Positive
MP	x is Medium Positive
S	x is small
MN	x is Medium Negative
LN	x is Large Negative

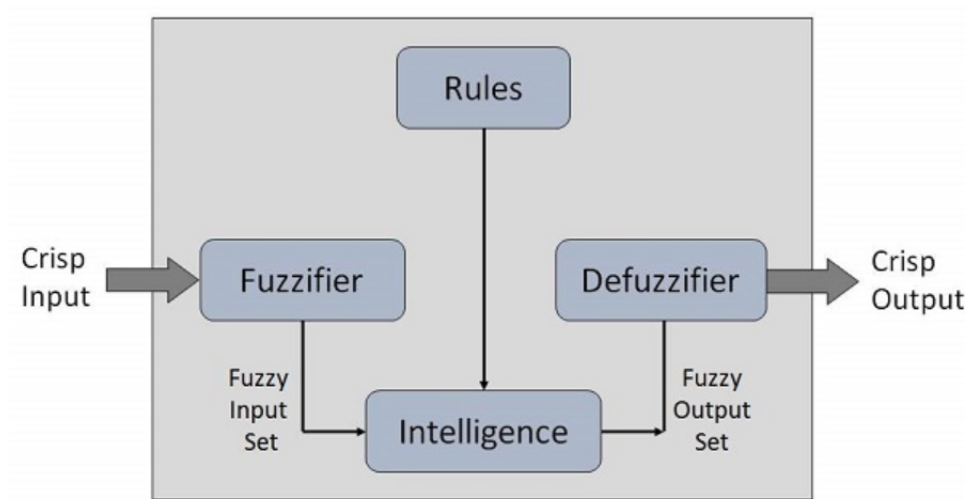- Knowledge Base:
 - It stores IF-THEN rules.
- Inference Engine:
 - it simulates the human reasoning process by making fuzzy inference on the inputs and IF-THEN.
- Defuzzification Module:
 - It transforms the fuzzy set obtained by the inference engine into crisp value.




11 Half Adder and Full Adder


- In digital system, an adder is a **digital circuit** in electronics that implies the addition of numbers.
- It is used in the arithmetic logic units. - It also utilizes the many parts of the processors, address, ... etc.

 11.1 Half Adder

- The half adder adds 2 binary inputs and produce the 2 outputs as SUM and CARRY; XOR gate is applied to both inputs to produce SUM; when AND gate is applied to produce CARRY.



Half Adder

 

Half Adder Logic Circuit

11.2 Full Adder

- The different between Full Adder and Half Adder is Full Adder use 3 binary inputs, which 2 of inputs can be referred as operands and the other one is a bit carried in.