

dce 2017




Review Midterm

Tran Ngoc Thinh
HCMC University of Technology
<http://www.cse.hcmut.edu.vn/~tnthinh>

BK TP.HCM

dce 2017


Overview

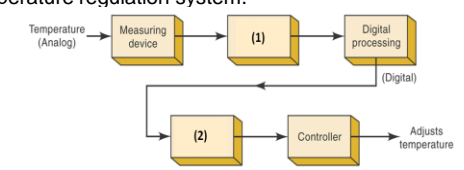- Choose the right answer to complete the diagram for a precision temperature regulation system.
 
 - (2) Digital-to-analog converter – (1) Analog-to-digital converter
 - (2) Analog-to-analog converter – (1) Digital-to-digital converter
 - (2) Digital-to-analog converter – (1) Analog-to-digital converter
 - (2) Analog-to-analog converter – (1) Digital-to-digital converter
- Which of the following is the most widely used alphanumeric code for computer input and output?
 - Gray
 - BCD
 - Parity
 - ASCII

BK TP.HCM

dce 2017


Boolean

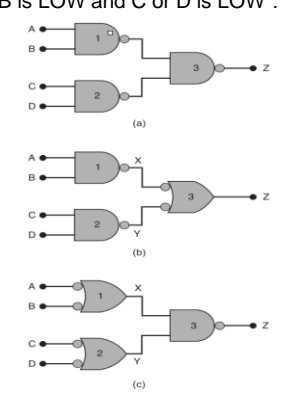- Which image is suitable the most with this description: "Output Z will go LOW only when A or B is LOW and C or D is LOW".
 - a
 - b
 - c
 - All of them

BK TP.HCM

dce 2017

Boolean

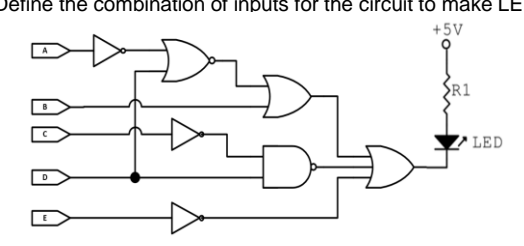- Define the combination of inputs for the circuit to make LED ON:
 
 - LED ON when $B = 0$ and $C = 0$ and $D = 1$ and $E = 1$
 - LED ON when $A = 1$ and $B = 0$ and $C = 0$ and $D = 0$ and $E = 1$
 - LED ON when $A = 0$ and $B = 0$ and $C = 0$ and $D = 1$ and $E = 0$
 - LED ON when $A = 1$ and $B = 0$ and $C = 1$ and $D = 0$ and $E = 0$

BK TP.HCM

Kmap

- Find the minimum Boolean function $F(ABC)$ in SOP form from the following k-map:

		BC			
		00	01	11	10
A	0	x	1	0	x
	1	1	x	x	1

- a. $F = AC' + B'$
 - b. $F = A + B$
 - c. $F = B' + C'$
 - d. Both b and c are true



Flip-flop

- The circuit that is primarily responsible for certain flip-flops to be designated as edge-triggered is the:

- A. NAND latch.
- B. NOR latch.
- C. pulse-steering circuit.
- D. edge-detection circuit.

- As a general rule for stable flip-flop triggering, the clock pulse rise and fall times must be:

- A. at a maximum value to enable the input control signals to stabilize.
- B. very long.
- C. of no consequence as long as the levels are within the determinate range of value.
- D. very short.



Flip-flop

- Edge-triggered flip-flops must have:


- A. active-low inputs and complemented outputs.
- B. a pulse transition or edge detector circuit.
- C. very fast response times.
- D. at least two inputs to handle rising and falling edges.

- What is one disadvantage of an S-R flip-flop?


- A. It has only a single output.
- B. It has no CLOCK input.
- C. It has no Enable input.
- D. It has an invalid state.



 
Problem: The waveforms below are to be applied to two different FF's. Draw Q for (a) positive edge-triggered (b) negative edge-triggered.



 
Problem: Compare the operation of the **D latch** with the **negative edge-triggered D FF** using the following waveforms.



Problem: Determine the Q output

 

 The signals A and B are applied to the inputs of an SR flip-flop (or Set-Clear FF), a transparent latch and a D-type flip-flop. Sketch the waveforms at W, X, Y and Z.



The circuit below is made from two D-type flip-flops with an asynchronous RESET input. Assume that Q0 and Q1 are both low initially and sketch a timing diagram showing the waveforms of CLOCK, Q0 and Q1 for the next six clock pulses.

