


dce 2018



Digital Systems

Chapter 2: Boolean Algebra & Logic Gates

BK TP.HCM

Tran Ngoc Thinh
HCMC University of Technology
<http://www.cse.hcmut.edu.vn/~tnthinh>

dce 2018

Boolean Constants and Variables

- Boolean algebra is an important tool in describing, analyzing, designing, and implementing digital circuits.
- Boolean algebra allows only two values; 0 and 1.
- Logic 0 can be: false, off, low, no, open switch.
- Logic 1 can be: true, on, high, yes, closed switch.
- Three basic logic operations: OR, AND, and NOT.

BK TP.HCM

2

dce 2018

Truth Tables

- A truth table describes the relationship between the input and output of a logic circuit.
- The number of entries corresponds to the number of inputs. For example a 2-input table would have $2^2 = 4$ entries. A 3-input table would have $2^3 = 8$ entries.

BK TP.HCM

3

dce 2018


Truth Tables

- Examples of truth tables with 2, 3, and 4 inputs.

Inputs Output

A	B	x
0	0	1
0	1	0
1	0	1
1	1	0

(a)

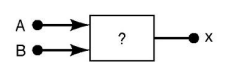

A	B	C	x
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

(b)

A	B	C	D	x
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

(c)


BK TP.HCM

4

OR Operation With OR Gates

- The Boolean expression for the OR operation is
 $X = A + B$
 - This is read as "x equals A or B."
 - $X = 1$ when $A = 1$ or $B = 1$.
- Truth table, circuit symbol and timing diagram for a two input OR gate:


A	B	$x = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

 

5

OR Operation With OR Gates

 - The OR operation is similar to addition but when $A = 1$ and $B = 1$, the OR operation produces $1 + 1 = 1$.
- In the Boolean expression
 $x = 1 + 1 + 1 + 1 = 1$
 We could say that x is true (1) when A is true (1) OR B is true (1) OR C is true (1) OR D is true (1).
- In general, the output of an **OR gate** is **HIGH** whenever **one or more inputs are HIGH**




A	B	C	D	X
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1



6

OR Operation With OR Gates

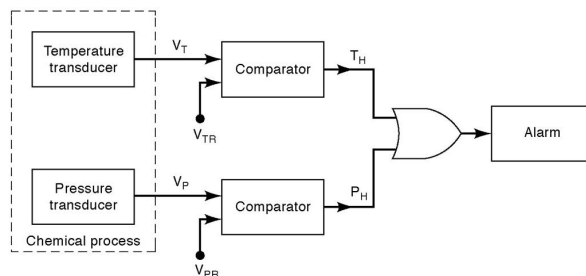- There are many examples of applications where an output function is desired when one of multiple inputs is activated.



7

Review Questions

- What is the only set of input conditions that will produce a LOW output for any OR gate?
 - all inputs LOW
- Write the Boolean expression for a six-input OR gate
 - $X = A + B + C + D + E + F$
- If the A input in previous example is permanently kept at the 1 level, what will the resultant output waveform be?
 - constant HIGH





8

AND Operations with AND gates

- The Boolean expression for the AND operation is

$$X = A \cdot B$$
 - This is read as "x equals A and B."
 - x = 1 when A = 1 and B = 1.
- Truth table and circuit symbol for a two input AND gate are shown. Notice the difference between OR and AND gates.

AND		
A	B	$x = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

  


AND Operation With AND Gates

- The AND operation is similar to multiplication.
- In the Boolean expression

$$X = A \cdot B \cdot C$$

$$X = 1 \text{ only when } A = 1, B = 1, \text{ and } C = 1.$$
- The output of an **AND gate** is **HIGH** only when **all inputs** are **HIGH**.

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

 

Review Questions

- What is the only input combination that will produce a HIGH at the output of a five-input AND gate?
 - all 5 inputs = 1
- What logic level should be applied to the second input of a two-input AND gate if the logic signal at the first input is to be inhibited(prevented) from reaching the output?
 - A LOW input will keep the output LOW
- True or false: An AND gate output will always differ from an OR gate output for the same input conditions.
 - False



NOT Operation

- The Boolean expression for the NOT operation is

$$X = \overline{A} \quad X = A'$$
- This is read as:
 - x equals NOT A, or
 - x equals the inverse of A, or
 - x equals the complement of A
- Truth table, symbol, and sample waveform for the NOT circuit.

NOT	
A	$x = \overline{A}$
0	1
1	0


(a)

  (b)
Presence of small circle always denotes inversion

(c)


Describing Logic Circuits Algebraically

 - The three basic Boolean operations (OR, AND, NOT) can describe any logic circuit.
- Examples of Boolean expressions for logic circuits:




Describing Logic Circuits Algebraically

 - The output of an inverter is equivalent to the input with a bar over it. Input A through an inverter equals A' .
- Examples using inverters.



More Examples

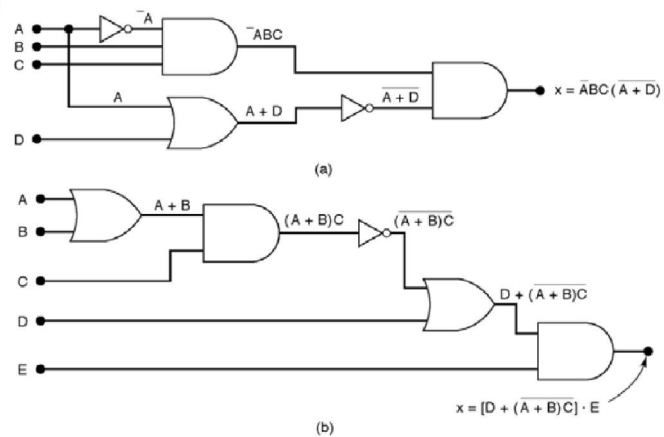

Evaluating Logic Circuit Outputs

- Rules for evaluating a Boolean expression:
 - Perform all inversions of single terms.
 - Perform all operations within parenthesis.
 - Perform AND operation before an OR operation unless parenthesis indicate otherwise.
 - If an expression has a bar over it, perform the operations inside the expression and then invert the result.

Evaluating Logic Circuit Outputs

- Evaluate Boolean expressions by substituting values and performing the indicated operations:

$A = 0, B = 1, C = 1, \text{ and } D = 1$


$$\begin{aligned} x &= \overline{A}BC(A + D) \\ &= \overline{0} \cdot 1 \cdot 1 \cdot \overline{(0 + 1)} \\ &= 1 \cdot 1 \cdot 1 \cdot \overline{(0 + 1)} \\ &= 1 \cdot 1 \cdot 1 \cdot \overline{1} \\ &= 1 \cdot 1 \cdot 1 \cdot 0 \\ &= 0 \end{aligned}$$



17

Evaluating Logic Circuit Outputs

 
- Output logic levels can be determined directly from a circuit diagram.
- Technicians frequently use this method.
- The output of each gate is noted until a final output is found.



18


Implementing Circuits From Boolean Expressions

 - It is important to be able to draw a logic circuit from a Boolean expression.
- The expression $x = A \cdot B \cdot C$



could be drawn as a three input AND gate.

- A more complex example such as

 

$y = AC + \overline{B}C + \overline{A}BC$ could be drawn as two 2-input AND gates and one 3-input OR gate feeding into a 3-input OR gate. Two of the AND gates have inverted inputs.




19

Example

- Draw the circuit diagram to implement the expression

$$x = (A + B)(\overline{B} + C)$$

 


20

Review Question

- Draw the circuit diagram that implements the expression


$$x = \overline{A}BC\overline{(A+D)}$$

 using gates having no more than three inputs.




NOR Gates and NAND Gates

 - Combine basic AND, OR, and NOT operations.
- The NOR gate is an inverted OR gate. An inversion "bubble" is placed at the output of the OR gate.
- The Boolean expression is $x = \overline{A+B}$



A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

 


NOR Gates and NAND Gates

- The NAND gate is an inverted AND gate. An inversion "bubble" is placed at the output of the AND gate.
- The Boolean expression is $x = \overline{AB}$



A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

 


Laws of Boolean Algebra


- Commutative Laws
- Associative Laws
- Distributive Laws

Commutative Laws of Boolean Algebra

$$A + B = B + A$$

 


$$A \cdot B = B \cdot A$$

 


Associative Laws of Boolean Algebra

$$A + (B + C) = (A + B) + C$$

 

 
$$A \cdot (B \cdot C) = (A \cdot B) \cdot C$$



Distributive Laws of Boolean Algebra

$$A \cdot (B + C) = A \cdot B + A \cdot C$$

$$A(B + C) = AB + AC$$

 

Rules of Boolean Algebra

- | | |
|----------------------|-------------------------------|
| 1. $A + 0 = A$ | 7. $A \cdot A = A$ |
| 2. $A + 1 = 1$ | 8. $A \cdot \bar{A} = 0$ |
| 3. $A \cdot 0 = 0$ | 9. $\bar{\bar{A}} = A$ |
| 4. $A \cdot 1 = A$ | 10. $A + AB = A$ |
| 5. $A + A = A$ | 11. $A + \bar{A}B = A + B$ |
| 6. $A + \bar{A} = 1$ | 12. $(A + B)(A + C) = A + BC$ |

dce 2018 Rules of Boolean Algebra

Rule 1: $X = A + 0 = A$

Rule 2: $X = A + 1 = 1$

Rule 3: $X = A \cdot 0 = 0$

Rule 4: $X = A \cdot 1 = A$

OR Truth Table

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

AND Truth Table

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

29

dce 2018 Rules of Boolean Algebra

Rule 5: $X = A + A = A$

Rule 6: $X = A + \bar{A} = 1$

Rule 7: $X = A \cdot A = A$

Rule 8: $X = A \cdot \bar{A} = 0$

OR Truth Table

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

AND Truth Table

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

30

dce 2018 Rules of Boolean Algebra

Rule 9: $\bar{\bar{A}} = A$

Rule 10: $A + AB = A$

AND Truth Table

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

OR Truth Table

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

31

dce 2018 Rules of Boolean Algebra

Rule 11: $A + A'B = A + B$

Rule 12: $(A + B)(A + C) = A + BC$

32

Examples

- Simplify the expression

$$y = A\bar{B}D + A\bar{B}\bar{D}$$

$$y = A\bar{B}$$

$$z = (\bar{A} + B)(A + B)$$

$$z = B$$

$$x = ACD + \bar{A}BCD$$

$$x = ACD + BCD$$

$$y = A\bar{C} + ABC\bar{C}$$

$$y = A\bar{C}$$



33

DeMorgan's Theorems

- Theorem 1: When the OR sum of two variables is inverted, it is equivalent to inverting each variable individually and ANDing them.

$$\overline{A + B} = \bar{A} \cdot \bar{B}$$

- Theorem 2: When the AND product of two variables is inverted, it is equivalent to inverting each variable individually and ORing them.

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$



34

DeMorgan's Theorems

- A NOR gate is equivalent to an AND gate with inverted inputs.
- A NAND gate is equivalent to an OR gate with inverted inputs.

For N variables, DeMorgan's theorem is expressed as:

$$\overline{ABC \dots N} = \bar{A} + \bar{B} + \bar{C} + \dots + \bar{N} \quad \text{and} \quad \overline{A + B + C + \dots + N} = \bar{A} \bar{B} \bar{C} \dots \bar{N}$$





Applying DeMorgan's theorem to the expression $\overline{ABC + DEF}$ we get:

$$\begin{aligned} \overline{ABC + DEF} &= (\overline{ABC}) (\overline{DEF}) \\ &= (\bar{A} + \bar{B} + \bar{C}) (\bar{D} + \bar{E} + \bar{F}) \end{aligned}$$



35


Implications of DeMorgan's Theorems

    

36

Implications of DeMorgan's Theorems

 - Determine the output expression for the below circuit and simplify it using DeMorgan's Theorem



- Use DeMorgan's theorems to convert below expression to an expression containing only single-variable inversions

$$y = \overline{A + \overline{B} + \overline{CD}}$$

$$y = \overline{A}B(C + \overline{D})$$



37

Example of DeMorgan's Theorems

$$F = \overline{XY} + \overline{P.Q}$$

$$F = \overline{X} + \overline{Y} + \overline{P} + \overline{Q}$$

- Simplify the expression
- $$z = \overline{(\overline{A} + C)(B + \overline{D})}$$
- to one having only single variables inverted.

$$z = A\overline{C} + \overline{B}D$$



38

Examples

- Simplify the expressions
- $$-z = (A' + B)(A+B)$$

- De Morgan's
- $$-z = ((a'+c) \cdot (b+d'))'$$



39

Examples

- Simplify the expressions

$$\begin{aligned} -z &= (A' + B)(A+B) \\ &= A'A + A'B + AB + BB = 0 + (A'+A)B + B = B \end{aligned}$$

- De Morgan's
- $$\begin{aligned} -z &= ((a'+c) \cdot (b+d'))' \\ &= (a'+c)' + (b+d')' = ac' + b'd \end{aligned}$$



40

Exercises

- Simplify the expressions

– a) $x = (M + N)(\overline{M} + P)(\overline{N} + \overline{P})$

– b) $z = \overline{A}B\overline{C} + A\overline{B}\overline{C} + \overline{B}C\overline{D}$

- De Morgan's


(a) $\overline{\overline{A}\overline{B}\overline{C}}$	(d) $\overline{\overline{A} + \overline{B}}$	(g) $\overline{\overline{A(B + \overline{C})D}}$
(b) $\overline{\overline{A} + \overline{B}C}$	(e) $\overline{\overline{A}B}$	(h) $\overline{(M + \overline{N})(\overline{M} + N)}$
(c) $\overline{\overline{A}B\overline{C}D}$	(f) $\overline{\overline{A} + \overline{C} + \overline{D}}$	(i) $\overline{\overline{A}B\overline{C}D}$



41


Universality of NAND and NOR Gates

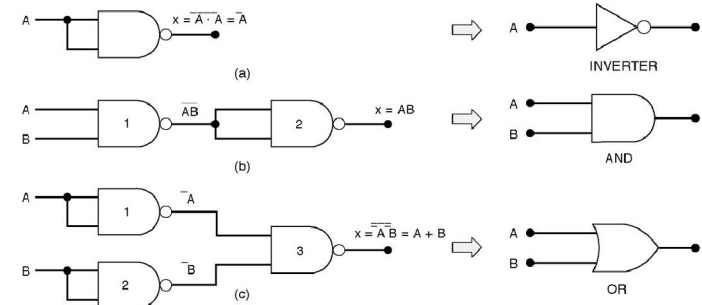- NAND or NOR gates can be used to create the three basic logic expressions (OR, AND, and INVERT)



42

Universality of NAND and NOR Gates

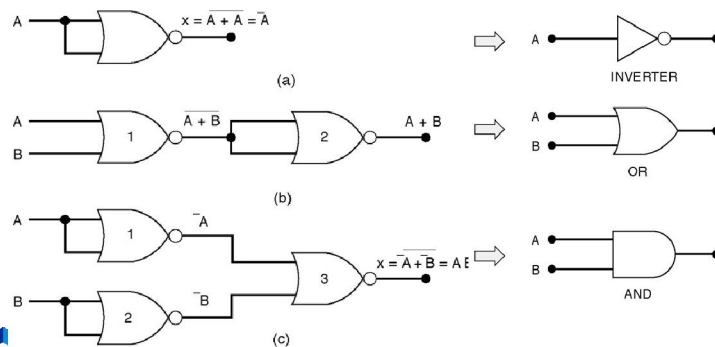

43

Alternate Logic-Gate Representations


- To convert a standard symbol to an alternate:
 - Invert each input and output (add an inversion bubble where there are none on the standard symbol, and remove bubbles where they exist on the standard symbol).
 - Change a standard OR gate to an AND gate, or an AND gate to an OR gate.



44

Alternate Logic-Gate Representations

 - Standard and alternate symbols for various logic gates and inverter



Alternate Logic-Gate Representations


- The equivalence can be applied to gates with any number of inputs.
- No standard symbols have bubbles on their inputs. All of the alternate symbols do.
- The standard and alternate symbols represent the same physical circuitry.

Alternate Logic-Gate Representations

- Active high – an input or output has no inversion bubble.
- Active low – an input or output has an inversion bubble.
- An AND gate will produce an active output when all inputs are in their active states.
- An OR gate will produce an active output when any input is in an active state.


Alternate Logic-Gate Representations

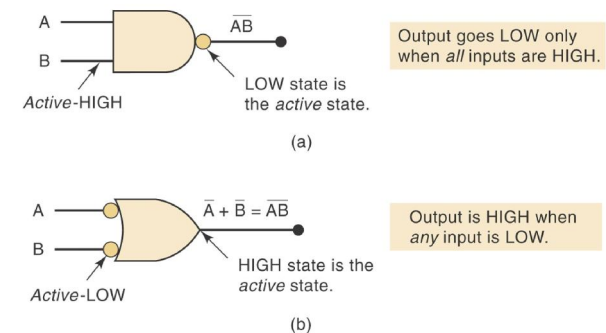- Interpretation of the two NAND gate symbols.




Alternate Logic-Gate Representations

 - Interpretation of the two OR gate symbols.



 Output goes HIGH when *any* input is HIGH.




Output goes LOW only when *all* inputs are LOW.

Which Gate Representation to Use

- Using alternate and standard logic gate symbols together can make circuit operation clearer.
- When possible choose gate symbols so that bubble outputs are connected to bubble input and nonbubble outputs are connected to nonbubble inputs.

Which Gate Representation to Use

 
- When a logic signal is in the active state (high or low) it is said to be **asserted**.
- When a logic signal is in the inactive state (high or low) it is said to be **unasserted**.
- A bar over a signal means asserted (active) low.
- The absence of a bar over a signal means asserted (active) high.



(a) Original circuit using standard NAND symbols; (b) equivalent representation where output Z is active-HIGH; (c) equivalent representation where output Z is active-LOW; (d) truth table.

A	B	C	D	Z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Example

 


Alarm is activated when Z goes high. Modify the circuit so that it represents the circuit operation more effectively.



53

 Example


Z activates another circuit when it goes low. Convert Z to Active-Low



54


Methods of describing logic circuits

 Boolean expression
warning_light = driver_present • buckled_up • ignition_on
(a)



Truth table

driver_present	buckled_up	ignition_on	warning_light
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

 


(a) Boolean expression;
(b) schematic diagram;
(c) truth table;
(d) timing diagram.



55

IEEE/ANSI Standard Logic Symbols

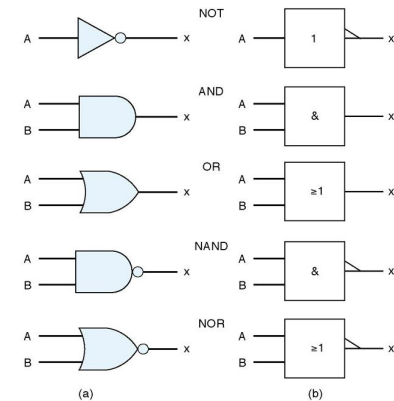- Rectangular symbols represent logic gates and circuits.
- Dependency notation inside symbols show how output depends on inputs.
- A small triangle replaces the inversion bubble.



56

- The three basic logic functions are AND, OR, and NOT.
- Logic functions allow us to represent a decision process.
 - If it is raining OR it looks like rain I will take an umbrella.
 - If I get paid AND I go to the bank I will have money to spend.



- Boolean Algebra: a mathematical tool used in the analysis and design of digital circuits
- OR, AND, NOT: basic Boolean operations
- OR: HIGH output when any input is HIGH
- AND: HIGH output only when all inputs are HIGH
- NOT: output is the opposite logic level as the input
- NOR: OR with its output connected to an INVERTER
- NAND: AND with its output connected to an INVERTER
- Boolean theorems and rules: to simplify the expression of a logic circuit and can lead to a simpler way of implementing the circuit
- NAND, NOR: can be used to implement any of the basic Boolean operations

