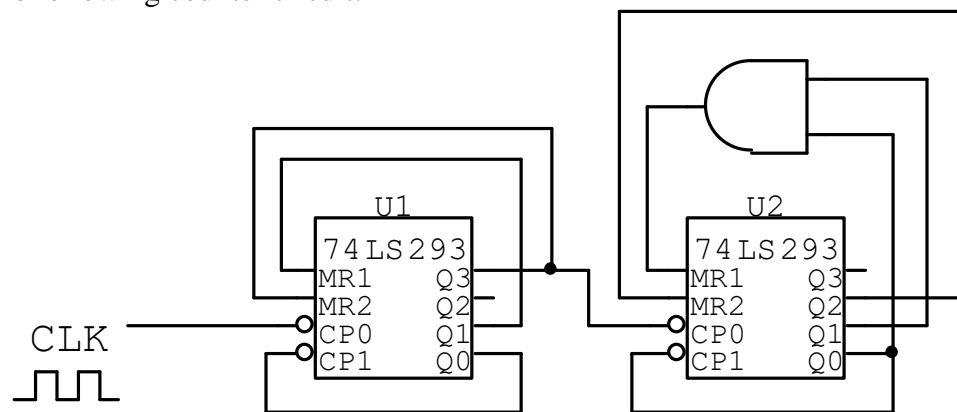



## COUNTERS & REGISTERS

1. Design a ripple counter, MOD-4, up counter, using J-K Flip-Flop and D Flip-Flop.
2. Design a ripple counter, MOD-12, up counter, using J-K Flip-Flop and D Flip-Flop.
3. (a) Design a ripple counter, MOD-16, down counter, using J-K Flip-Flop and D Flip-Flop.  
(b) Suppose the counter is in state 0110, determine the state of the counter after the next 27 clock cycles.
4. Design a ripple counter, MOD-5, down counter, using J-K Flip-Flop and D Flip-Flop..
5. Use J-K Flip-Flop and D Flip-Flop to design an asynchronous counter as follows:  
$$4 \rightarrow 5 \rightarrow 6 \rightarrow 7 \rightarrow 4 \rightarrow \dots$$
6. Use J-K Flip-Flop and D Flip-Flop to design an asynchronous down counter as follows  
$$6 \rightarrow 5 \rightarrow 4 \rightarrow 3 \rightarrow 2 \rightarrow 1 \rightarrow 6 \rightarrow \dots$$
7. Given the following counter circuit:




With the frequency of the clock signal  $f_{CLK} = 35 \text{ KHz}$

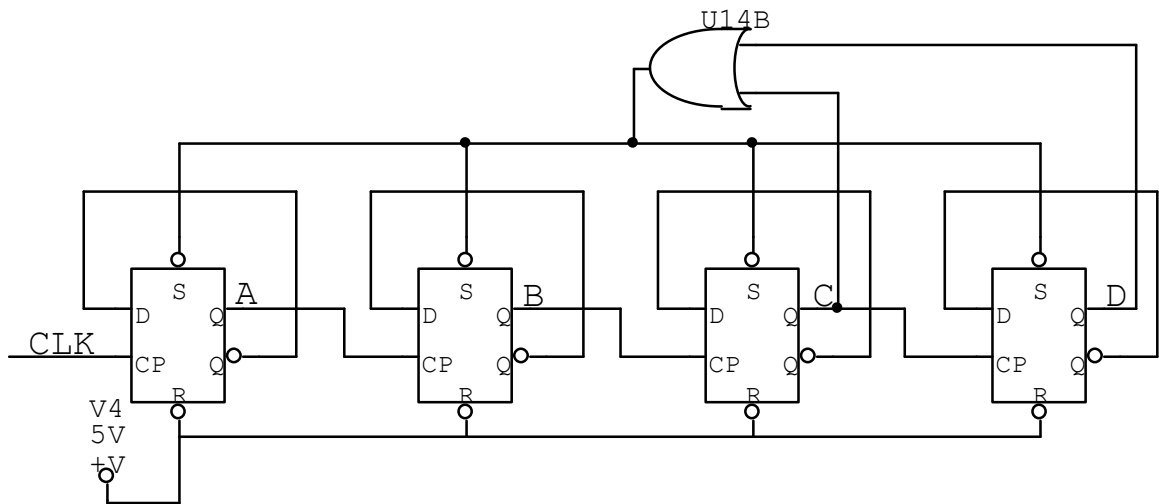- (a) What is the MOD of the counter?
  - (b) Determine the frequency of Q3 of U1?
  - (c) Determine the frequency of Q2 of U2?
  - (d) In the Q3, Q2, Q1, Q0 signals of U1 and U2, which signals are glitches?
  - (e) Determine duty cycle of Q2 of U2?
- 8.** Given the following counter circuit:




- What is the MOD of the counter?
- In the A, B, C, D signals, which signals are glitches?
- What is the frequency of output B as compared with the frequency of CLK?
- What is the frequency of output D as compared with the frequency of CLK?

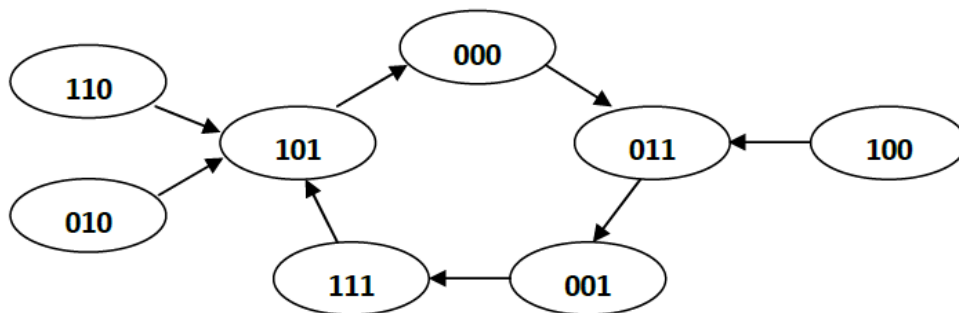
9. Use J-K Flip-Flop to design a synchronous counter circuits according to the following transition diagram:



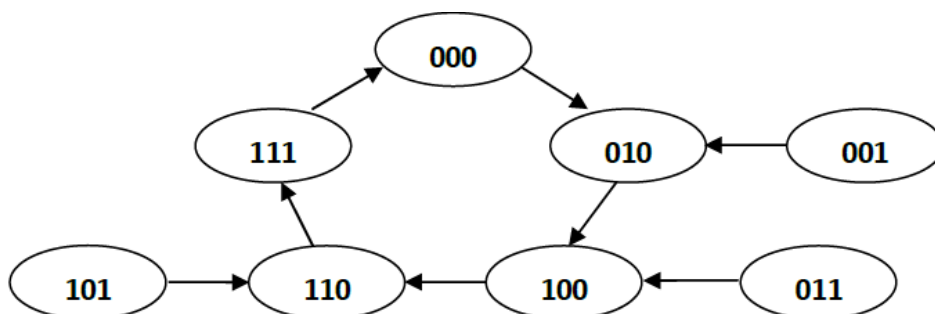
10. Use D-FlipFlop to design a synchronous counter circuits according to the following transition diagram:



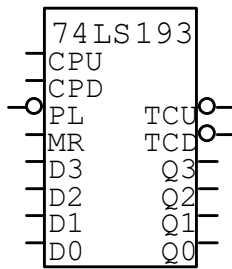11. Use 74LS193 and 74LS32 ICs to design a down counter from 12  $\rightarrow$  5




12. Given the following counter circuit:

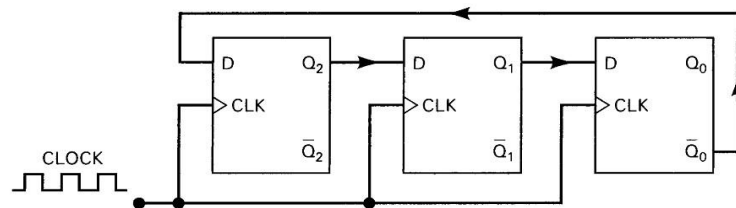


Assume the initial state of the counter  $Q_2Q_1Q_0 = 000$ , determine the sequence of the counter.

13. Given the following counter circuit

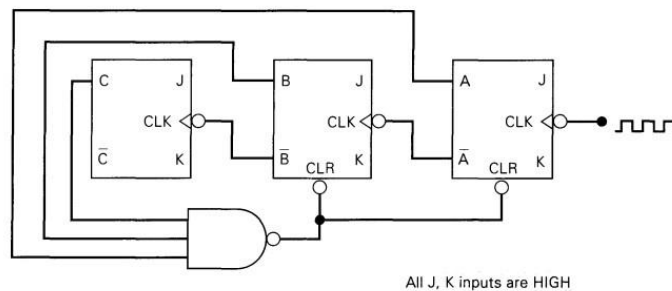

Assume the initial state of the counter  $CBA = 010$ , determine the sequence of the counter.

14. Given the following counter circuit:

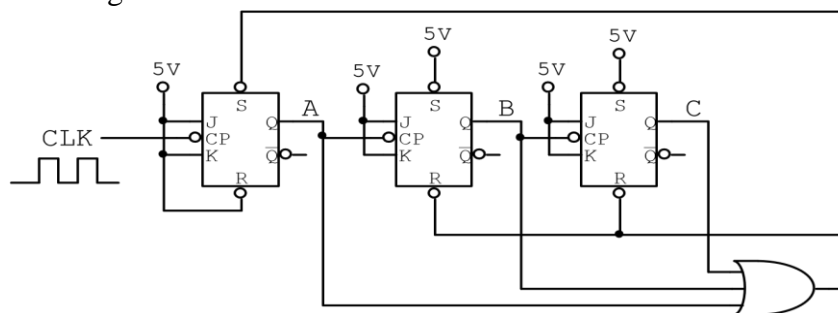

Assume the initial state of the counter  $CBA = 010$ , determine the sequence of the counter.