



DIGITAL SYSTEMS REPORT

LAB 05

Group 1

No.	Name	ID
1	Vo Dong Ho	1752219
2	Nguyen Minh Nhat	1752039
3	Huynh Gia An Tien	1752538
4	Pham Minh Tuan	1752595

Table of Contents

1	Contents	5
2	Exercises	6
2.1	Exercise 1	7
2.2	Exercise 2	10
2.3	Exercise 3	12
2.4	Exercise 4	13
2.5	Exercise 5	16
2.6	Exercise 6	22
2.7	Exercise 7	26
2.8	Exercise 8	29

Content

Question 1. *Distinguish between Combinational circuit and Sequential circuit.*

- A combinational circuit has no memory characteristic, so its output depends only on the current value of its inputs.
- A sequential circuit is one in which the outputs follow a predetermined sequence of states, with a new state occurring each time a clock pulse occurs.

Question 2.

- *How can you declare a negative triggered edge in sensitive list?*
- *In the example, assume that*

$$\begin{cases} out1 = 5 \\ out2 = 0 \\ in = 1 \end{cases}$$

What is the value of and out2 in the clock trigger? Explain your results? Answer: out1 = 0 and out2 = 5 - since the assignments are non-blocking assignments.

- *In the above example, we are using rst to reset the output value. This kind of reset is called synchronous reset. You have to change the code to describe an asynchronous reset.*

```
1 always @ (posedge clk or posedge rst)
2   begin
3     if (rst)
4       begin
5         out1 <= 0;
6         out2 <= 0;
7       end
8     else
9       begin
10        if (in == 1)
11          begin
12            out1 <= out2;
13            out2 <= out1;
14          end
15        else
16          begin
17            out1 <= out1 + 1;
18            out2 <= 0;
19          end
20        end
21      end
```

Exercises

The module `seven_seg.v` (7seg-led decoder) is used in most exercises.

```
1 module seven_seg(  
2     seg,  
3     bcd  
4 );  
5  
6     output [6:0] seg;  
7     input  [3:0] bcd;  
8  
9     assign seg = (bcd == 4'd0) ? 7'b1000000  
10                : (bcd == 4'd1) ? 7'b1111001  
11                : (bcd == 4'd2) ? 7'b0100100  
12                : (bcd == 4'd3) ? 7'b0110000  
13                : (bcd == 4'd4) ? 7'b0011001  
14                : (bcd == 4'd5) ? 7'b0010010  
15                : (bcd == 4'd6) ? 7'b0000011  
16                : (bcd == 4'd7) ? 7'b1111000  
17                : (bcd == 4'd8) ? 7'b0000000  
18                : (bcd == 4'd9) ? 7'b0011000  
19                : /* undefined */ 7'b1111111;  
20  
21 endmodule
```

Exercise 1.

Implement D FF and JK FF

1. D FF


- Function table:

R	CLK	D	Q	Q'
0	X	X	0	1
1	\uparrow	0	0	1
1	\uparrow	1	1	0


- Verilog:

```
1 module d_ff(  
2     q, q_n,  
3     clk, d, rst_n  
4 );  
5  
6     output q, q_n;  
7     reg    q;  
8     input  clk,  
9           d,  
10          rst_n;  
11  
12     always @ (posedge clk or negedge rst_n)  
13     begin  
14         if (!rst_n)  
15             q <= 0;  
16         else  
17             q <= d;  
18     end  
19  
20     assign q_n = ~q;  
21  
22 endmodule
```

- Waveform:

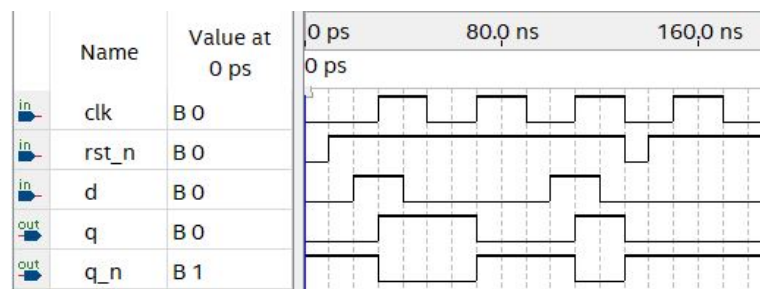

- Generated Circuit:

 

2. JK FF


- Function table:

\overline{PRE}	\overline{CLR}	CLK	J	K	Q
1	1	\downarrow	0	0	Q (no change)
1	1	\downarrow	0	1	0 (synch reset)
1	1	\downarrow	1	0	1 (synch set)
1	1	\downarrow	1	1	\overline{Q} (synch toggle)
1	1	X	X	X	Q (no change)
1	0	X	X	X	0 (asynch clear)
0	1	X	X	X	1 (asynch preset)
0	0	X	X	X	(invalid)


- Verilog:

```
1 module jk_ff(  
2     q, q_n,  
3     pre_n, clr_n,  
4     clk_n,  
5     j, k  
6 );  
7  
8     output q,  
9         q_n;  
10    reg    q;  
11    input  pre_n,  
12         clr_n,  
13         clk_n,  
14         j,  
15         k;  
16  
17    always @ (negedge clk_n or negedge pre_n or negedge clr_n)  
18        begin  
19            if (!pre_n)  
20                q <= 1;  
21            else if (!clr_n)  
22                q <= 0;  
23            else  
24                if (j)  
25                    if (k)  
26                        q <= ~q;  
27                    else  
28                        q <= 1;  
29                else  
30                    if (k)  
31                        q <= 0;  
32            end  
33  
34    assign q_n = ~q;  
35  
36 endmodule
```

- Waveform:

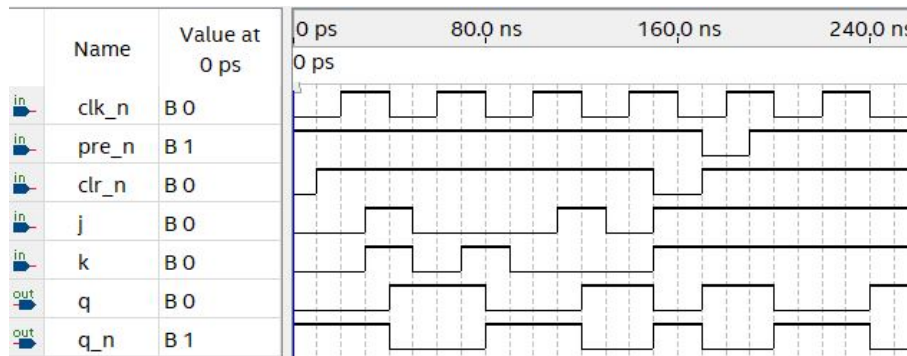

- Generated Circuit:

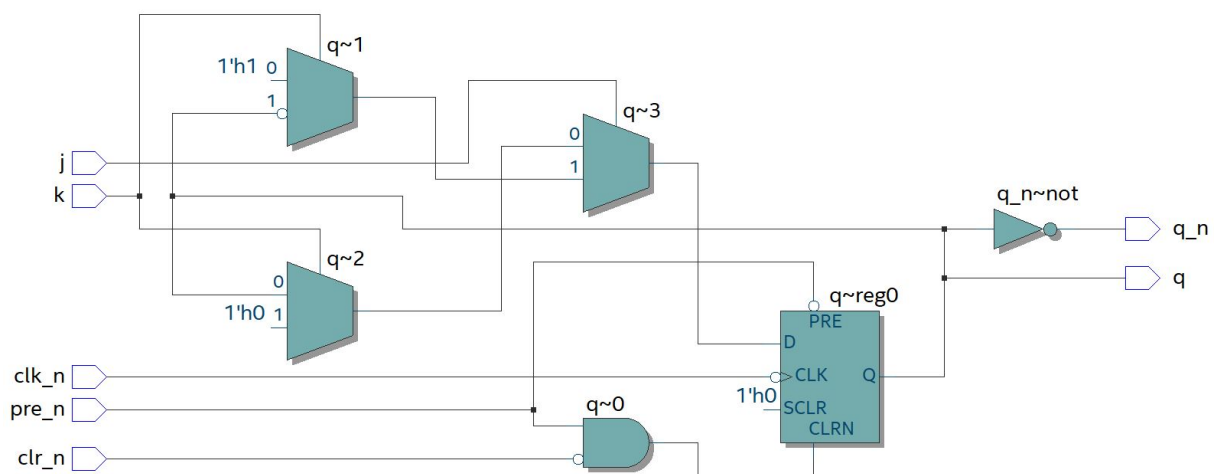

Exercise 2.

Implement a shift 4-bit circuit by using 4 D FF.


- Design

- The output Q of the previous D FF is connected to the input D of the next FF.
- One common CLK signal is used for all FFs.


- Verilog Code

```
1 module four_bit_shift_reg(  
2     out,  
3     clk,  
4     data  
5 );  
6  
7     output [3:0] out;  
8     input  clk,  
9         data;  
10  
11     d_ff d_ff_0(  
12         .q(out[0]),  
13         .clk(clk),  
14         .d(data),  
15         .rst_n(1)  
16     );  
17  
18     d_ff d_ff_1(  
19         .q(out[1]),  
20         .clk(clk),  
21         .d(out[0]),  
22         .rst_n(1)  
23     );  
24  
25     d_ff d_ff_2(  
26         .q(out[2]),  
27         .clk(clk),  
28         .d(out[1]),  
29         .rst_n(1)  
30     );  
31  
32     d_ff d_ff_3(  
33         .q(out[3]),  
34         .clk(clk),  
35         .d(out[2]),  
36         .rst_n(1)  
37     );  
38  
39 endmodule
```

- Waveform

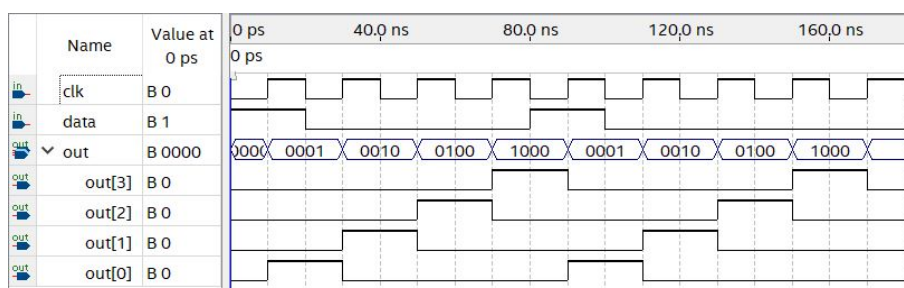

- Generated Circuit

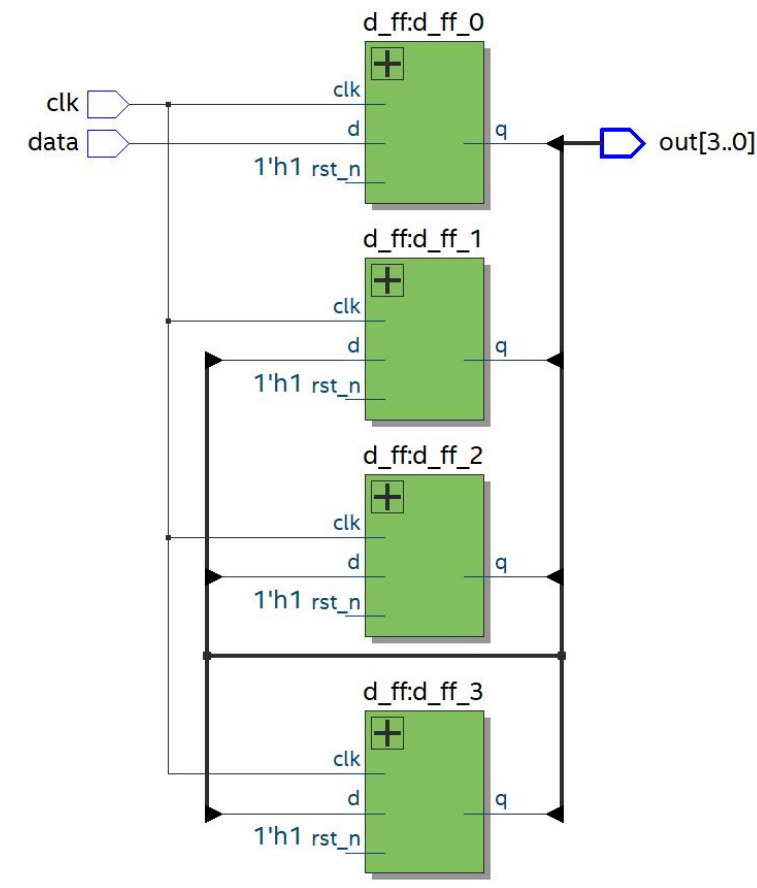

Exercise 3.

Design clock divider circuit provided a 50 MHz clock.

- **Design**

- The frequency is reduced by half for each D FF it passes through.
- For an input frequency of 50MHz, to obtain the output frequency of 1Hz (1 led blink per second), there needs to be:

$$\lceil \log_2(50 \cdot 10^6) \rceil = 26 \quad (DFF)$$

- The output Q of the previous D FF is the CLK signal of the next FF.
- Each time a D FF is clock-triggered, it "toggles" itself. D FFs do not have the built-in toggle function like JK FFs, but we can obtain the same functionality by connecting the D input of one FF to its inverted output \overline{Q} .

- **Verilog Code**


```
1 module clk_divider(  
2     fout,  
3     fin  
4 );  
5  
6     output fout;  
7     wire [26:0] f;  
8     input fin;  
9  
10    assign f[0] = fin;  
11  
12    genvar i;  
13    generate  
14        for (i = 1; i <= 26; i = i + 1)  
15            begin : d_ff_label  
16                d_ff d_ff(  
17                    .q(f[i]),  
18                    .q_n(),  
19                    .d(~f[i]),  
20                    .clk(f[i - 1]),  
21                    .rst_n(1)  
22                );  
23            end  
24    endgenerate  
25  
26    assign fout = f[26];  
27  
28 endmodule
```

Exercise 4.

Implement a synchronous counter mod 8 which can count Up/Down by using JK FF and show the result on 7seg-led.

– Design

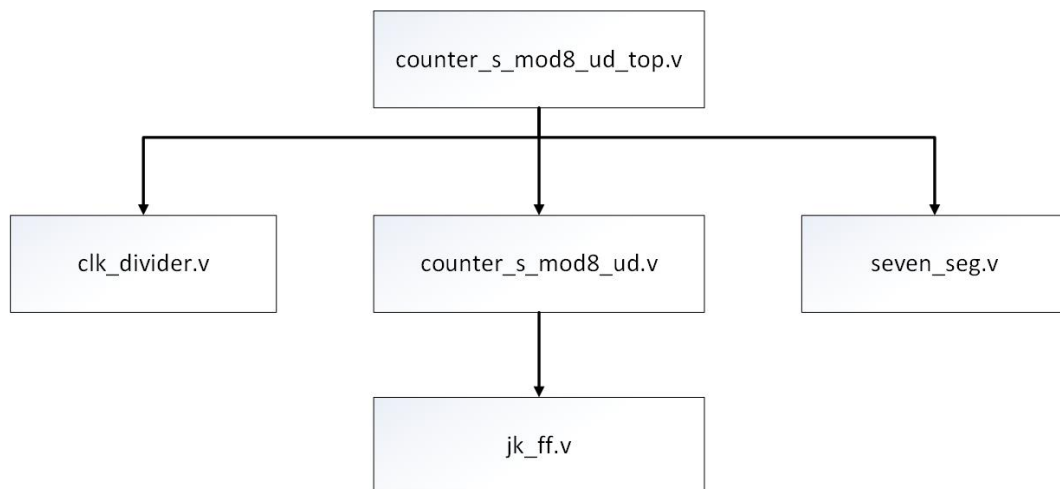- * Since the counter is synchronous, each JK FF has the same CLK signal.
- * If UP is 1, then the counter counts up. Otherwise, it counts down.
- * If the counter counts up, each FF toggles when all outputs of previous FFs are 1s.
- * If the counter counts down, each FF toggles when all outputs of previous FFs are 0s.
- * Hierarchical design:



– Verilog Code

```
1 module counter_s_mod8_ud(  
2     out,  
3     up,  
4     clk  
5 );  
6  
7     output [2:0] out;  
8     input  up,  
9         clk;  
10    wire  [2:1] in;  
11    wire  [2:1] and_wire;  
12    wire  [2:1] and_wire_n;  
13  
14    // FF 0  
15    jk_ff jk_ff_0(  
16        .q(out[0]),  
17        .pre_n(1),  
18        .clr_n(1),  
19        .j(1),  
20        .k(1),  
21        .clk_n(clk)  
22    );  
23  
24    // FF 1  
25    and and_gate_1(  
26        and_wire[1],  
27        up, out[0]  
28    );
```

```

29
30     and and_gate_n_1(
31         and_wire_n[1],
32         ~up, ~out[0]
33     );
34
35     or or_gate_1(
36         in[1],
37         and_wire[1], and_wire_n[1]
38     );
39
40     jk_ff jk_ff_1(
41         .q(out[1]),
42         .pre_n(1),
43         .clr_n(1),
44         .j(in[1]),
45         .k(in[1]),
46         .clk_n(clk)
47     );
48
49     // FF 2
50     and and_gate_2(
51         and_wire[2],
52         up, out[0], out[1]
53     );
54
55     and and_gate_n_2(
56         and_wire_n[2],
57         ~up, ~out[0], ~out[1]
58     );
59
60     or or_gate_2(
61         in[2],
62         and_wire[2], and_wire_n[2]
63     );
64
65     jk_ff jk_ff_2(
66         .q(out[2]),
67         .pre_n(1),
68         .clr_n(1),
69         .j(in[2]),
70         .k(in[2]),
71         .clk_n(clk)
72     );
73
74 endmodule

```

```

1 module counter_s_mod8_ud_top(
2     seg,
3     raw_clk,
4     up
5 );
6
7     output [6:0] seg;
8     input raw_clk;
9     input up;
10
11     wire clk;
12     wire [2:0] counter_out;
13
14     clk_divider clk_divider(
15         .fout(clk),
16         .fin(raw_clk)


```

```


17 );
18
19 counter_s_mod8_ud counter(
20     .out(counter_out),
21     .up(up),
22     .clk(clk)
23 );
24
25 seven_seg seven_seg(
26     .bcd(counter_out),
27     .seg(seg)
28 );
29
30 endmodule

```

– Waveform

 

– Generated Circuit

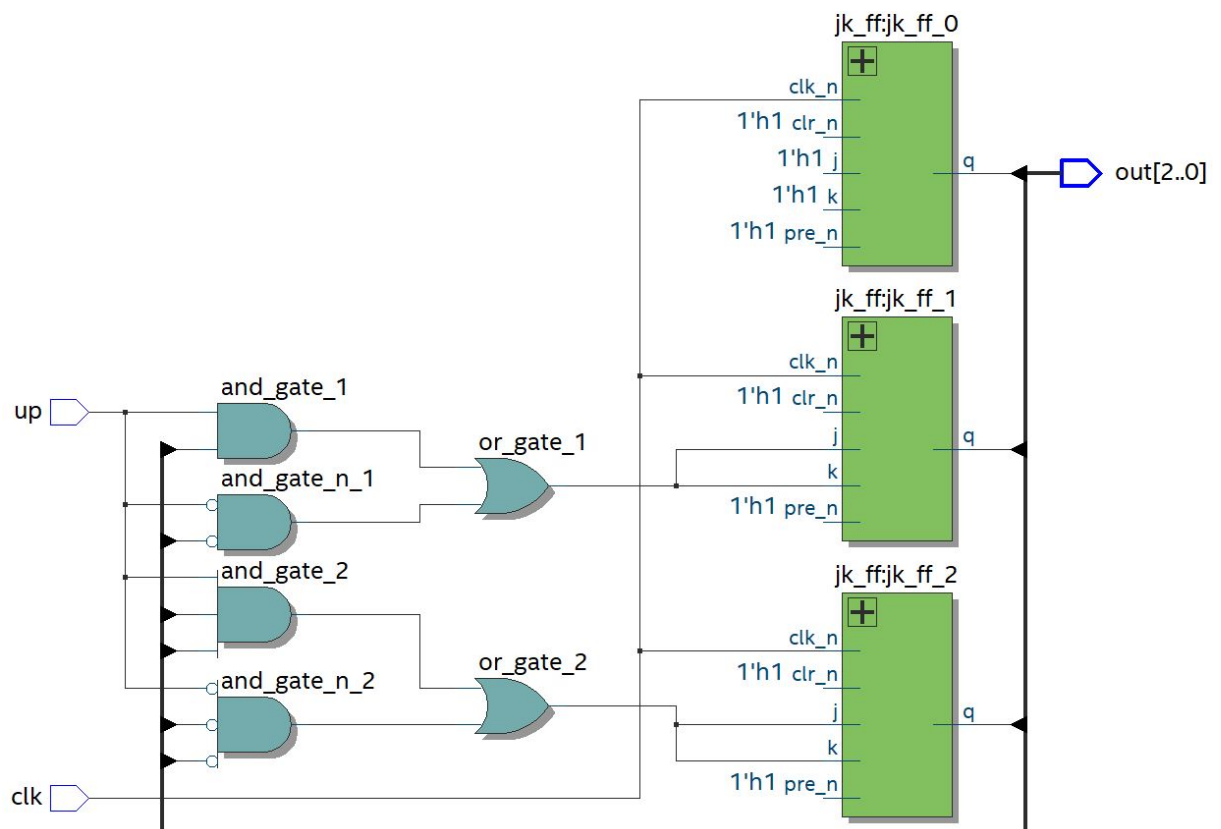

Exercise 5.

Implement a synchronous counter mod 11 by using D FF with the rule: 0 1 3 5 2 4 6 7 14 10 11 0... show the result on 7seg-led bonus if you use JK FF instead of D FF.

– Design

Using JK FFs.


- * Since the counter is synchronous, each JK FF has the same CLK signal.
- * A *CLR* signal is added to the counter to set initial state for waveform.
- * To design the synchronous counter with special rule, we need to take these steps:

1. Determined the number of FFs needed.

Since the largest number is $14 < 16 = 2^4$, 4 FFs are used.

 2. Draw the state diagram of the counter, including all used and unused states.

Used states are full circles; unused states are dashed circles.



3. Create the present state - next state table

	Previous State	Next State
0	0000	0001
1	0001	0011
2	0010	0100
3	0011	0101
4	0100	0110
5	0101	0010
6	0110	0111
7	0111	1110
8	1000	0000
9	1001	0000
10	1010	1011
11	1011	0000
12	1100	0000
13	1101	0000
14	1110	1010
15	1111	0000

4. For each PRESENT state, determine the required J and K input in order to produce the transition to the NEXT state.

	Present state	J_3	K_3	J_2	K_2	J_1	K_1	J_0	K_0
0	0000	0	X	0	X	0	X	1	X
1	0001	0	X	0	X	1	X	X	0
2	0010	0	X	1	X	X	1	0	X
3	0011	0	X	1	X	X	1	X	0
4	0100	0	X	X	0	1	X	0	X
5	0101	0	X	X	1	1	X	X	1
6	0110	0	X	X	0	X	0	1	X
7	0111	1	X	X	0	X	0	X	1
8	1000	X	1	0	X	0	X	0	X
9	1001	X	1	0	X	0	X	X	1
10	1010	X	0	0	X	X	0	1	X
11	1011	X	1	0	X	X	1	X	1
12	1100	X	1	X	1	0	X	0	X
13	1101	X	1	X	1	0	X	X	1
14	1110	X	0	X	1	X	0	0	X
15	1111	X	1	X	1	X	1	X	1

5. Simplify each J and K with Kmap or algebraically.

Final result after simplifying with Kmap:

$$J_0 = \bar{A}\bar{B}\bar{C} + \bar{A}BC + A\bar{B}C$$

$$K_0 = A + B$$

$$J_1 = \bar{A}B + \bar{A}D$$

$$K_1 = \bar{A}\bar{B} + AD$$

$$J_2 = \bar{A}C$$


$$K_2 = A + \bar{C}D$$

$$J_3 = BCD$$

$$K_3 = \bar{C} + D$$

where A is the MSB.

* Hierarchical design:

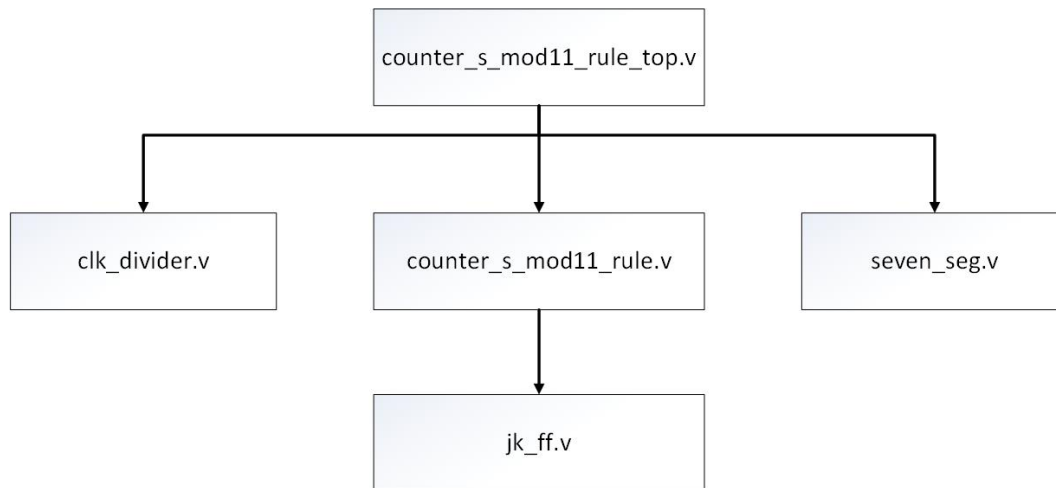

– Verilog Code

```
1 module counter_s_mod11_rule(
2     out,
3     clk,
4     clr_n,
5 );
6
7     output [3:0] out;
8     input  clk,
9           clr_n;
10
11     wire    [3:0] j;
12     wire    [3:0] k;
13
14     /***** Wire assignment *****/
15     wire    a, b, c, d;
16     assign a = out[3];
17     assign b = out[2];
18     assign c = out[1];
19     assign d = out[0];
20
21     /***** FF Inputs *****/
22     assign j[0] = (~a & ~b & ~c) | (~a & b & c) | (a & ~b & c);
23     assign k[0] = (a) | (b);
24     assign j[1] = (~a & b) | (~a & d);
25     assign k[1] = (~a & ~b) | (a & d);
26     assign j[2] = (~a & c);
27     assign k[2] = (a) | (~c & d);
28     assign j[3] = (b & c & d);
29     assign k[3] = (~c) | (d);
30
31     /***** FFs *****/
32     jk_ff jk_ff_0(
33         .q(out[0]),
34         .pre_n(1),
35         .clr_n(clr_n),
36         .clk_n(clk),
37         .j(j[0]),
38         .k(k[0])
39     );
40
41     jk_ff jk_ff_1(
42         .q(out[1]),
43         .pre_n(1),
44         .clr_n(clr_n),
45         .clk_n(clk),
46         .j(j[1]),
47         .k(k[1])
48     );
49
50     jk_ff jk_ff_2(
51         .q(out[2]),
52         .pre_n(1),
53         .clr_n(clr_n),
54         .clk_n(clk),
55         .j(j[2]),
56         .k(k[2])
57     );
58
59     jk_ff jk_ff_3(
60         .q(out[3]),
61         .pre_n(1),
```

```

62     .clr_n(clr_n),
63     .clk_n(clk),
64     .j(j[3]),
65     .k(k[3])
66 );
67
68 endmodule


```

```


1  module counter_s_mod11_rule_top(
2      seg,
3      raw_clk,
4      clr_n
5  );
6
7      output [13:0] seg;
8      input  raw_clk;
9      input  clr_n;
10     wire    clk;
11     wire    [3:0] counter_out;
12     wire    [3:0] unit_bcd;
13     wire    [3:0] tenth_bcd;
14
15     clk_divider clk_divider(
16         .fout(clk),
17         .fin(raw_clk)
18     );
19
20     counter_s_mod11_rule counter(
21         .out(counter_out),
22         .clk(clk),
23         .clr_n(clr_n)
24     );
25
26     assign unit_bcd = (counter_out > 4'd9) ? (counter_out - 10)
27                                     : (counter_out);
28     assign tenth_bcd = (counter_out > 4'd9) ? (1) : (0);
29
30     seven_seg seven_seg_0(
31         .bcd(unit_bcd),
32         .seg(seg[6:0])
33     );
34
35     seven_seg seven_seg_1(
36         .bcd(tenth_bcd),
37         .seg(seg[13:7])
38     );
39
40 endmodule

```

– Waveform

 

– Generated Circuit

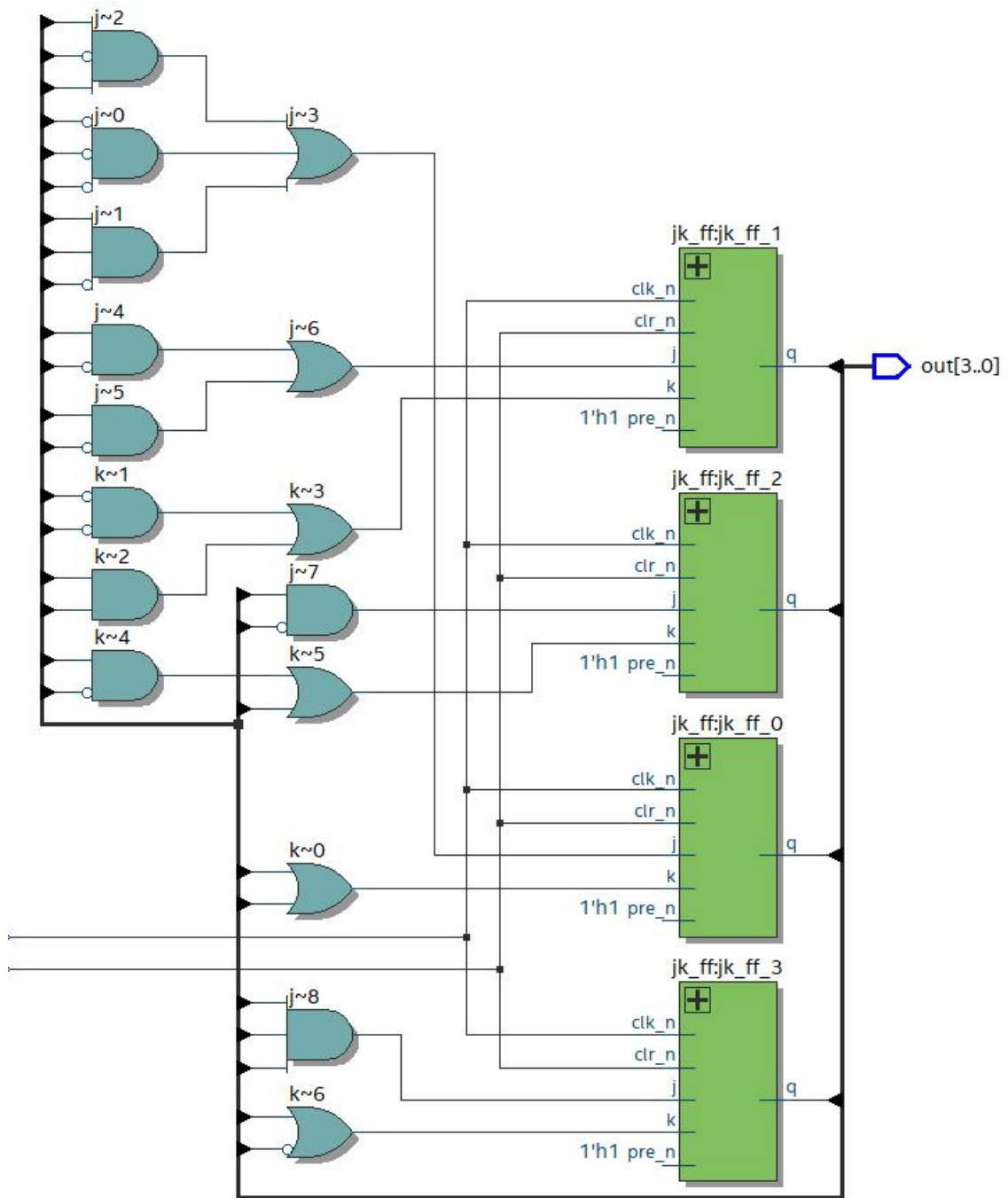


Exercise 6.

Implement 4 bit Synchronous counter with asynchronous parallel load.

– **Design**

FF type: JK

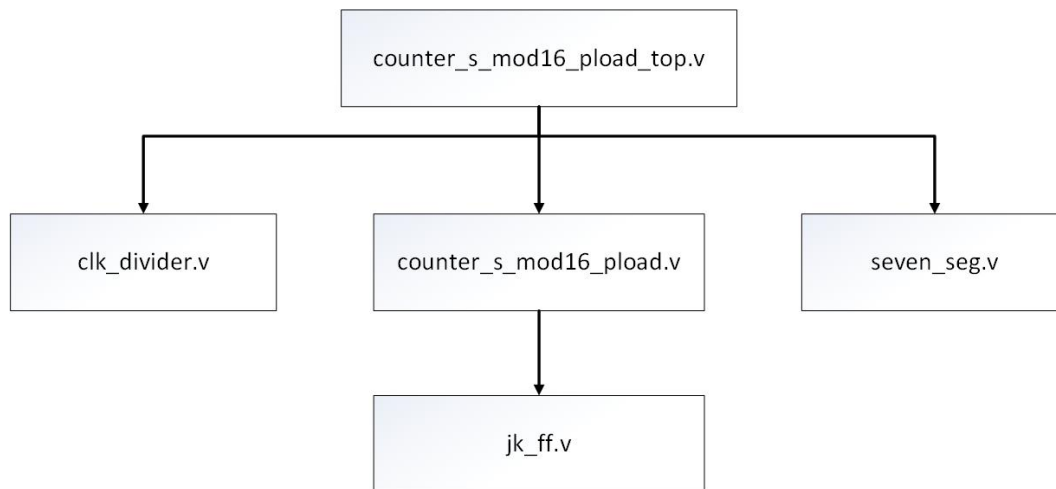- * Since the counter is synchronous, each JK FF has the same CLK signal.
- * Use the RTL branching structure, we can assign the suitable value for *PRE* and *CLR* when *PL* is active:
 - If *DATA* = 1, then *PRE* = 0 and *CLR* = 1.
 - If *DATA* = 0, then *PRE* = 1 and *CLR* = 0.
- * Hierarchical design:



– Verilog Code

```
1 module counter_s_mod16_pload(
2   out,
3   clk,
4   data,
5   pl_n
6 );
7
8   output [3:0] out;
9   input  clk;
10  input  [3:0] data;
11  input  pl_n;
12
13  wire    [3:0] pre_n;
14  wire    [3:0] clr_n;
15  wire    [3:1] j;
16  wire    [3:1] k;
17
18  assign pre_n[0] = (!pl_n) ? (~data[0]) : (1);
19  assign clr_n[0] = (!pl_n) ?  (data[0]) : (1);
20  assign pre_n[1] = (!pl_n) ? (~data[1]) : (1);
21  assign clr_n[1] = (!pl_n) ?  (data[1]) : (1);
22  assign pre_n[2] = (!pl_n) ? (~data[2]) : (1);
23  assign clr_n[2] = (!pl_n) ?  (data[2]) : (1);
24  assign pre_n[3] = (!pl_n) ? (~data[3]) : (1);
25  assign clr_n[3] = (!pl_n) ?  (data[3]) : (1);
26
27  jk_ff jk_ff_0(
28    .q(out[0]),
29    .pre_n(pre_n[0]),
30    .clr_n(clr_n[0]),
31    .clk_n(clk),
32    .j(1),
33    .k(1)
34  );
35
36  assign j[1] = out[0];
37  assign k[1] = out[0];
38
39  jk_ff jk_ff_1(
40    .q(out[1]),
41    .pre_n(pre_n[1]),
42    .clr_n(clr_n[1]),
43    .clk_n(clk),
44    .j(j[1]),
45    .k(k[1])
46  );
47
48  assign j[2] = out[0] & out[1];
49  assign k[2] = out[0] & out[1];
50
51  jk_ff jk_ff_2(
52    .q(out[2]),
53    .pre_n(pre_n[2]),
54    .clr_n(clr_n[2]),
55    .clk_n(clk),
56    .j(j[2]),
57    .k(k[2])
58  );
59
60  assign j[3] = out[0] & out[1] & out[2];
61  assign k[3] = out[0] & out[1] & out[2];
```

```


62
63     jk_ff jk_ff_3(
64         .q(out[3]),
65         .pre_n(pre_n[3]),
66         .clr_n(clr_n[3]),
67         .clk_n(clk),
68         .j(j[3]),
69         .k(k[3])
70     );
71
72 endmodule

```


```

1  module counter_s_mod16_pload_top(
2      seg,
3      raw_clk,
4      data,
5      pl_n
6  );
7
8      output [13:0] seg;
9      input  raw_clk;
10     input  [3:0] data;
11     input  pl_n;
12     wire   clk;
13     wire   [3:0] counter_out;
14     wire   [3:0] unit_bcd;
15     wire   [3:0] tenth_bcd;
16
17     clk_divider clk_divider(
18         .fout(clk),
19         .fin(raw_clk)
20     );
21
22     counter_s_mod16_pload counter(
23         .out(counter_out),
24         .clk(clk),
25         .data(data),
26         .pl_n(pl_n)
27     );
28
29     assign unit_bcd = (counter_out > 4'd9) ? (counter_out - 4'd10) : (
        counter_out);
30     assign tenth_bcd = (counter_out > 4'd9) ? (4'd1) : (4'd0);
31
32     seven_seg seven_seg_0(
33         .bcd(unit_bcd),
34         .seg(seg[6:0])
35     );
36
37     seven_seg seven_seg_1(
38         .bcd(tenth_bcd),
39         .seg(seg[13:7])
40     );
41
42 endmodule

```

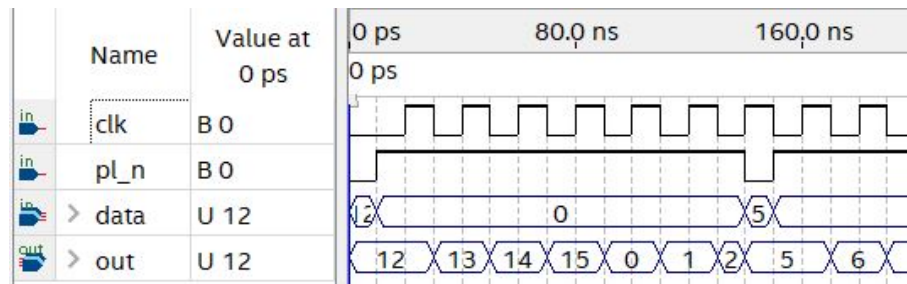

– Generated Circuit

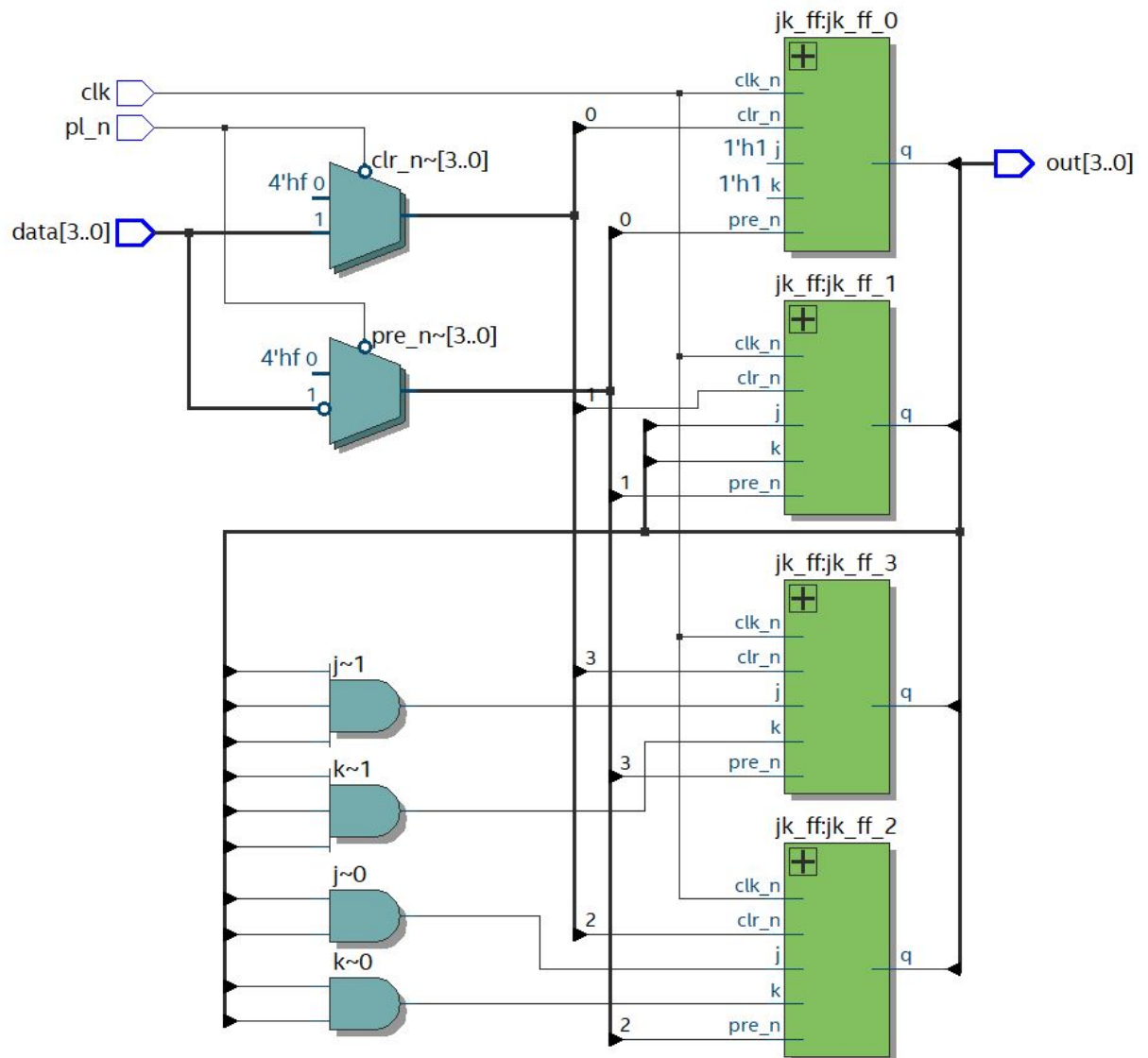


Exercise 7.

Implement an asynchronous counter mod 8 by using D FF and show the result on 7seg-led.

– Design

- * The counter is asynchronous. Therefore, to correctly implement the counter, we have to take into account propagation delay.
- * Each time a D FF is clocked-triggered, it toggles itself. This result is obtained by connecting each FF's input D to its inverted output \bar{Q} .
- * The CLK signal of a D FF is the inverted output of the previous FF. Because of that, any D FF (except the first one) would toggle twice as slow as the previous one.
- * Hierarchical design:

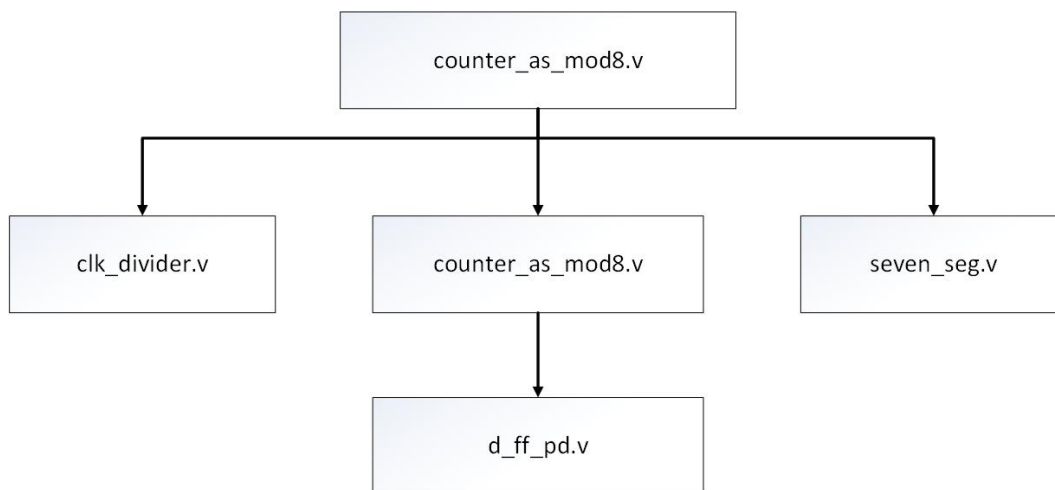

– Verilog Code

```
1 module d_ff_pd(  
2     q,  
3     clk, d, rst_n  
4 );  
5  
6     output q;  
7     reg    q_nodelay;  
8     input  clk,  
9           d,  
10          rst_n;  
11  
12     always @ (posedge clk or negedge rst_n)  
13     begin  
14         if (!rst_n)  
15             q_nodelay <= 0;  
16         else  
17             q_nodelay <= d;  
18     end  
19  
20     assign #2 q = q_nodelay;  
21  
22 endmodule
```

```
1 module counter_as_mod8(  
2     out,  
3     clk,  
4     rst_n
```

```

5 );
6
7     output [2:0] out;
8     input  clk,
9           rst_n;
10
11     d_ff_pd d_ff_0(
12         .q(out[0]),
13         .rst_n(rst_n),
14         .clk(clk),
15         .d(~out[0])
16     );
17
18     d_ff_pd d_ff_1(
19         .q(out[1]),
20         .rst_n(rst_n),
21         .clk(~out[0]),
22         .d(~out[1])
23     );
24
25     d_ff_pd d_ff_2(
26         .q(out[2]),
27         .rst_n(rst_n),
28         .clk(~out[1]),
29         .d(~out[2])
30     );
31
32 endmodule


```

```


1 module counter_as_mod8_top(
2     seg,
3     raw_clk,
4     rst_n
5 );
6
7     output [6:0] seg;
8     input  raw_clk;
9     input  rst_n;
10
11     wire  clk;
12     wire  [2:0] clk_out;
13
14     clk_divider clk_divider(
15         .fout(clk),
16         .fin(raw_clk)
17     );
18
19     counter_as_mod8 counter(
20         .out(clk_out),
21         .clk(clk),
22         .rst_n(rst_n)
23     );
24
25     seven_seg seven_seg(
26         .seg(seg),
27         .bcd(clk_out)
28     );
29
30 endmodule

```

– Waveform

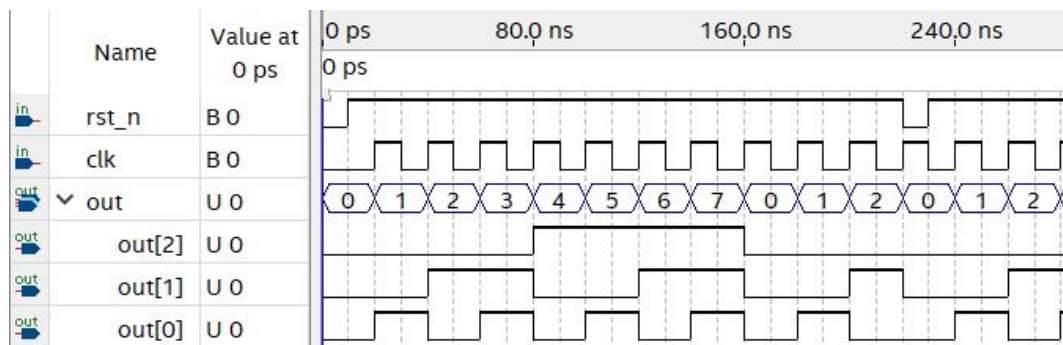

– Generated Circuit

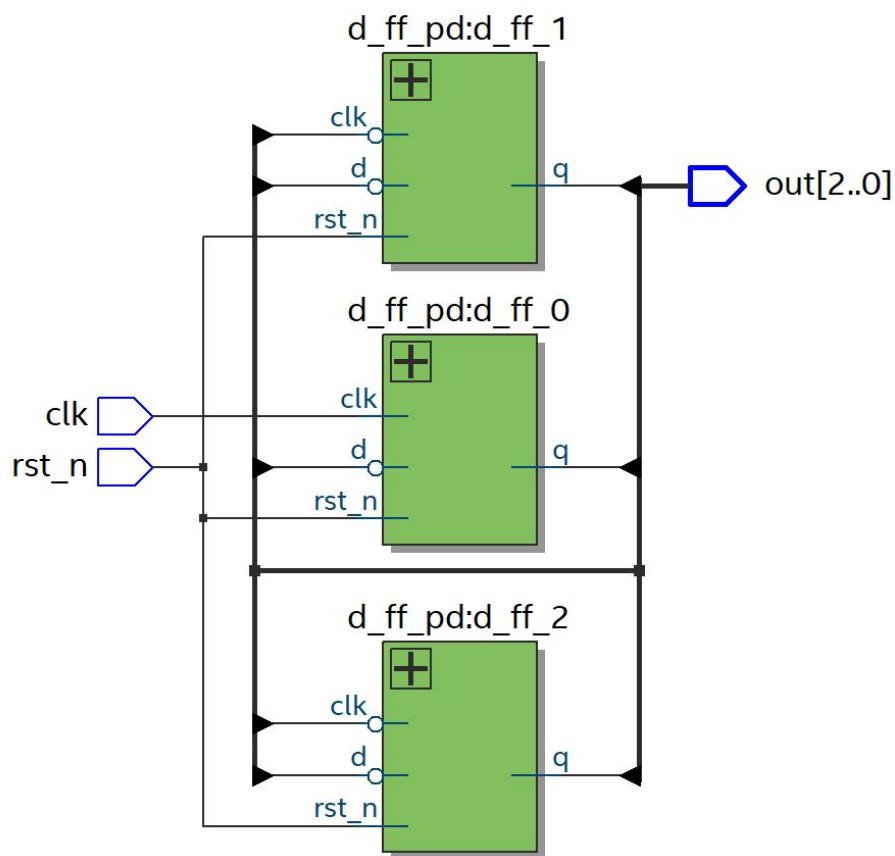


Exercise 8.

Implement an asynchronous counter mod 14 by using JK FF and show the result on 7seg-led.

– Design

- * Similar to exercise 7, since the counter is asynchronous, we have to take into account propagation delay.
- * J and K are always kept at 1. Each time a JK FF is clocked-triggered, it toggles itself.
- * To reset at 14, A NAND gate which has
 - Inputs: all signals that are 1 at number 14.
 - Output: the common CLR signal of all JK FF.
- * There is a manual reset signal to stabilize the initial state of the counter.
- * Hierarchical design:

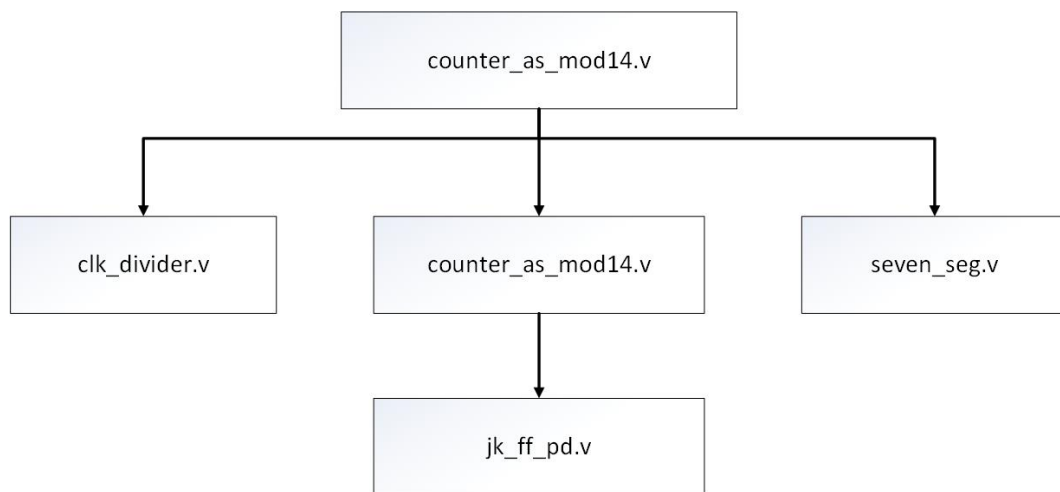

– Verilog Code

```
1 module jk_ff_pd(  
2     q,  
3     pre_n, clr_n,  
4     clk_n,  
5     j, k  
6 );  
7  
8     output q;  
9     reg    q_nodelay;  
10    input  pre_n,  
11          clr_n,  
12          clk_n,  
13          j,  
14          k;  
15  
16    always @ (negedge clk_n or negedge pre_n or negedge clr_n)  
17    begin  
18        if (!pre_n)  
19            q_nodelay <= 1;  
20        else if (!clr_n)  
21            q_nodelay <= 0;  
22        else  
23            if (j)  
24                if (k)  
25                    q_nodelay <= ~q_nodelay;
```

```

26         else
27             q_nodelay <= 1;
28         else
29             if (k)
30                 q_nodelay <= 0;
31         end
32
33     assign #2 q = q_nodelay;
34
35 endmodule

```

```

1 module counter_as_mod14(
2     out,
3     clk,
4     m_clr_n
5 );
6
7     output [3:0] out;
8     input  clk,
9           m_clr_n;
10
11     wire  clr_n;
12
13     assign clr_n = m_clr_n & ~(out[3] & out[2] & out[1]); // 14 == 1110
14
15     jk_ff_pd jk_ff_0(
16         .q(out[0]),
17         .pre_n(1),
18         .clr_n(clr_n),
19         .clk_n(clk),
20         .j(1),
21         .k(1)
22     );
23
24     jk_ff_pd jk_ff_1(
25         .q(out[1]),
26         .pre_n(1),
27         .clr_n(clr_n),
28         .clk_n(out[0]),
29         .j(1),
30         .k(1)
31     );
32
33     jk_ff_pd jk_ff_2(
34         .q(out[2]),
35         .pre_n(1),
36         .clr_n(clr_n),
37         .clk_n(out[1]),
38         .j(1),
39         .k(1)
40     );
41
42     jk_ff_pd jk_ff_3(
43         .q(out[3]),
44         .pre_n(1),
45         .clr_n(clr_n),
46         .clk_n(out[2]),
47         .j(1),
48         .k(1)
49     );
50
51 endmodule


```

```

1 module counter_as_mod14_top(
2     seg,
3     raw_clk,
4     clr_n
5 );
6
7     output [13:0] seg;
8     input  raw_clk;
9     input  clr_n;
10
11     wire  clk;
12     wire [3:0] counter_out;
13     wire [3:0] unit_bcd;
14     wire [3:0] tenth_bcd;
15
16     clk_divider clk_divider(
17         .fout(clk),
18         .fin(raw_clk)
19     );
20
21     counter_as_mod14 counter(
22         .out(counter_out),
23         .clk(clk),
24         .m_clr_n(clr_n)
25     );
26
27     assign unit_bcd = (counter_out > 4'd9) ? (counter_out - 4'd10)
28                                     : (counter_out);
29     assign tenth_bcd = (counter_out > 4'd9) ? (4'd1) : (4'd0);
30
31     seven_seg seven_seg_0(
32         .bcd(unit_bcd),
33         .seg(seg[6:0])
34     );
35
36     seven_seg seven_seg_1(
37         .bcd(tenth_bcd),
38         .seg(seg[13:7])
39     );
40
41 endmodule

```

– Waveform

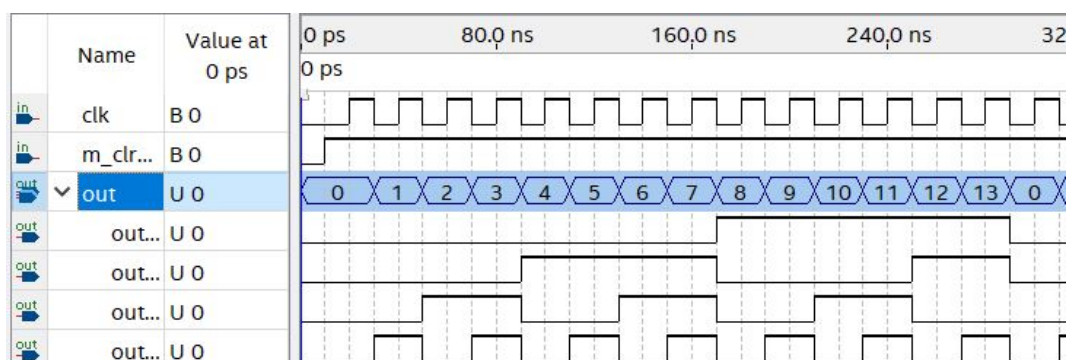

– Generated Circuit

