

Digital Systems

Chapter 3b: Introduction to Verilog

Tran Ngoc Thinh

Adapted from Dr. Pham Quoc Cuong's slides (cuongpham@hcmut.edu.vn) and Prof. Mike Schulte's slides (schulte@engr.wisc.edu)
Computer Engineering – CSE – HCMUT



1

Overview of HDLs

- Hardware description languages (HDLs)
 - Are computer-based hardware **description** languages
 - Allow modeling and simulating the functional behavior and timing of digital hardware
 - Synthesis tools take an HDL description and generate a technology-specific netlist
- Two main HDLs used by industry
 - Verilog HDL (C-based, industry-driven) (**60% of US companies use it**)
 - VHSIC HDL or VHDL (Ada-based, defense/industry/university-driven).



2

Synthesis of HDLs

- Takes a description of what a circuit DOES
- Creates the hardware to DO it
- HDLs may LOOK like software, **but they're not!**
 - NOT a program
 - Doesn't "run" on anything
 - Though we do *simulate* them on computers
 - Don't confuse them!
- Also use HDLs to test the hardware you create
 - This is more like software




3

Describing Hardware!

- All hardware created during synthesis
 - Even if a is true, still computing d&e
- Learn to understand how descriptions translated to hardware
 
```
if (a) f = c & d;  
else if (b) f = d;  
else f = d & e;
```



4

Why Use an HDL?

- More and more transistors can fit on a chip
 - Allows larger designs!
 - Work at transistor/gate level for large designs: hard
 - Many designs need to go to production quickly
- Abstract large hardware designs!
 - Describe what you need the hardware to do
 - Tools then design the hardware for you



5

Why Use an HDL?

- Simplified & faster design process
- Explore larger solution space
 - Smaller, faster, lower power
 - Throughput vs. latency
 - Examine more design tradeoffs
- Lessen the time spent debugging the design
 - Design errors still possible, but in fewer places
 - Generally easier to find and fix
- Can reuse design to target different technologies
 - Don't manually change all transistors for rule change



6

Other Important HDL Features

- Are highly portable (text)
- Are self-documenting (when commented well)
- Describe multiple levels of abstraction
- Represent parallelism
- Provides many descriptive styles
 - Structural
 - Register Transfer Level (RTL)
 - Behavioral
- Serve as input for synthesis tools



7

Verilog

- In this class, we will use the Verilog HDL
 - Used in academia and industry
- VHDL is another common HDL
 - Also used by both academia and industry
- Many principles we will discuss apply to any HDL
- Once you can “think hardware”, you should be able to use any HDL fairly quickly




8

Verilog Modules

```

1  module AOI_str (y_out, x_in1, x_in2, x_in3,
2    x_in4, x_in4);
3
4    output y_out;
5    input x_in1, x_in1, x_in2, x_in3,
6      x_in4, x_in4;
7
8    wire y1, y2;
9
10   nor (y_out, y1, y2);
11   and (y1, x_in1, x_in2);
12   and (y2, x_in3, x_in4, x_in5);
13 endmodule

```

 

Advanced Digital Design
with the Verilog HDL -
chapter 4

Verilog Module

- In Verilog, a circuit is a **module**.
 - A *module* is the building block in Verilog.
 - It is declared by the keyword *module* and is always terminated by the keyword *endmodule*.
 - Each statement is terminated with a semicolon, but there is no semi-colon after *endmodule*.


```

module module_name ( port_list );
  port declarations;
  ...
  variable declaration;
  ...
  description of behavior
endmodule

```

10

Verilog Module

 

module name

module smpl_circuit(A,B,C,x,y);

port types

input A,B,C;

output x,y;

wire e;

module contents

and g1(e,A,B);

not g2(y,C);

or g3(x,e,y);

endmodule

keywords underlined

11

Verilog Module (2)

module name

ports names of module

port types

module decoder_2_to_4 (A, D);

input [1:0] A;

output [3:0] D;

port sizes

assign D =

(A == 2'b00) ? 4'b0001 :

(A == 2'b01) ? 4'b0010 :

(A == 2'b10) ? 4'b0100 :

(A == 2'b11) ? 4'b1000 ;

module contents

endmodule

keywords underlined

12

Declaring A Module

- Can't use keywords as module/port/signal names
 - Choose a *descriptive* module name
- Indicate the ports (connectivity)
- Declare the signals connected to the ports
 - Choose *descriptive* signal names
- Declare any internal signals
- Write the internals of the module (functionality)



13

Declaring Ports

- A signal is attached to every port
- Declare type of port
 - **input**
 - **output**
 - **inout** (bidirectional)
- Scalar (single bit) - don't specify a size
 - **input** cin;
- Vector (multiple bits) - specify size using range
 - Range is MSB to LSB (left to right)
 - Don't have to include zero if you don't want to... (**D[2:1]**)
 - **output** **[7:0]** OUT;
 - **input** **[1:0]** IN;



14

Module Styles

- Modules can be specified different ways
 - Structural – connect primitives and modules
 - RTL – use continuous assignments
 - Behavioral – use initial and always blocks
- A single module can use more than one method!
- What are the differences?



15

Structural

- A schematic in text form
- Build up a circuit from gates/flip-flops
 - Gates are primitives (part of the language)
 - Flip-flops themselves described behaviorally
- Structural design
 - Create module interface
 - Instantiate the gates in the circuit
 - Declare the internal wires needed to connect gates
 - Put the names of the wires in the correct port locations of the gates
 - For primitives, outputs always come first



16

Structural Example

```
module majority (major, V1, V2, V3);
```


```
output major;
input V1, V2, V3;
```

```
wire N1, N2, N3;
```

```
and A0 (N1, V1, V2),
     A1 (N2, V2, V3),
     A2 (N3, V3, V1);
```

```
or Or0 (major, N1, N2, N3);
```

```
endmodule
```

 

17


RTL Example

```
module majority (major, V1, V2, V3);
```

```
output major;
input V1, V2, V3;
```

```
assign major = V1 & V2
               | V2 & V3
               | V1 & V3;
```

```
endmodule
```

 

18


Behavioral Example

```
module majority (major, V1, V2, V3);
```

```
output reg major;
input V1, V2, V3;
```

```
always @(V1, V2, V3) begin
    if (V1 && V2 || V2 && V3
        || V1 && V3) major = 1;
    else major = 0;
end
```

```
endmodule
```

 


19

Description Styles

- **Structural:** Logic is described in terms of Verilog gate primitives

 - Example:

```
not n1(sel_n, sel);
and a1(sel_b, b, sel_b);
and a2(sel_a, a, sel);
or o1(out, sel_b, sel_a);
```




20

Description Styles (cont.)

- **Dataflow (RTL):** Specify output signals in terms of input signals

- Example:

```
assign out = (sel & a) | (~sel & b);
```

 


Description Styles (cont.)

- **Behavioral:** Algorithmically specify the behavior of the design

 - Example:

```
if (select == 0) begin
    out = b;
end
else if (select == 1) begin
    out = a;
end
```



Structural Basics: Primitives

- Build design up from the gate/flip-flop/latch level
 - Flip-flops actually constructed using Behavioral
- Verilog provides a set of gate primitives
 - and, nand, or, nor, xor, xnor, not, buf, bufif1, etc.
 - Combinational building blocks for structural design
 - Known “behavior”
 - Cannot access “inside” description
- Can also model at the transistor level
 - Most people don’t, we won’t



23

Primitives

- No declarations - can only be instantiated
- Output port appears before input ports
- Optionally specify: instance name and/or delay (discuss delay later)

```
and N25 (Z, A, B, C); // name specified
and #10 (Z, A, B, X),
        (X, C, D, E); // delay specified, 2 gates
and #10 N30 (Z, A, B); // name and delay specified
```




24

Verilog Primitives

- 26 pre-defined primitives
- Output is the first port

| n-input | n-output 3-states |
|---------|----------------------|
| and | buf |
| nand | not |
| or | bufif0 |
| nor | bufif1 |
| xor | notif0 |
| xnor | notif1 |

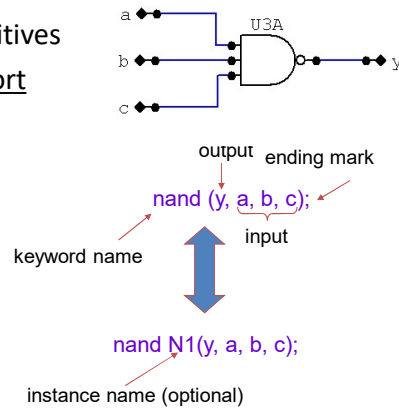

25

Syntax For Structural Verilog


- First declare the interface to the module
 - Module keyword, module name
 - Port names/types/sizes
- Next, declare any internal wires using “wire”
 - wire [3:0] partialsum;
- Then *instantiate* the primitives/submodules
 - Indicate which signal is on which port



26

Verilog - Module

 - A *module* is the building block in Verilog.
- It is declared by the keyword *module* and is always terminated by the keyword *endmodule*.
- Each statement is terminated with a semicolon, but there is no semi-colon after *endmodule*.



Verilog – Module (2)

HDL Example

```

module smpl_circuit (A,B,C,x,y);
    input  A,B,C;
    output x,y;
    wire  e;
    and    g1(e,A,B);
    not    g2(y,C);
    or     g3(x,e,y);
endmodule
    
```



Again: Structural Example

```
module majority (major, V1, V2, V3) ;
```


```
output major ;
input V1, V2, V3 ;
```

```
wire N1, N2, N3;
```

```
and A0 (N1, V1, V2),
     A1 (N2, V2, V3),
     A2 (N3, V3, V1);
```

```
or Or0 (major, N1, N2, N3);
```


```
endmodule
```

 

29

 Example

- Using the Verilog structural style, describe the following circuit



30

Example (1)

```
module example2 (x1, x2, x3, x4, f, g, h);
```

```
input x1, x2, x3, x4;
```

```
output f, g, h;
```

```
and (z1, x1, x3);
```

```
and (z2, x2, x4);
```

```
or (g, z1, z2);
```


```
or (z3, x1, ~x3);
```

```
or (z4, ~x2, x4);
```

```
and (h, z3, z4);
```

```
or (f, g, h);
```

```
endmodule
```

 

Example: Combinational Gray code

$$S_2' = \overline{Rst} S_2 S_0 + \overline{Rst} S_1 \overline{S_0}$$

$$S_1' = \overline{Rst} \overline{S_2} S_0 + \overline{Rst} S_1 \overline{S_0}$$

$$S_0' = \overline{Rst} \overline{S_2} \overline{S_1} + \overline{Rst} S_2 S_1$$



32

Datatypes

- Two categories
 - Nets
 - “Registers”
- Only dealing with nets in structural Verilog
- “Register” datatype doesn’t actually imply an actual register...
 - Will discuss this when we discuss Behavioral Verilog



33

Net Types

- **Wire**: most common, establishes connections
 - Default value for all signals
- **Tri**: indicates will be output of a tri-state
 - Basically same as “wire”
- **supply0, supply1**: ground & power connections
 - Can imply this by saying “0” or “1” instead
 - xor xorgate(out, a, 1'b1);
- **wand, wor, triand, trior, tri0, tri1, trireg**
 - Perform some signal resolution or logical operation
 - Not used in this course



34

Structural Verilog: Connections

- “Positional” or “Implicit” port connections
 - Used for primitives (first port is output, others inputs)
 - Can be okay in some situations
 - Designs with very few ports
 - Interchangeable input ports (and/or/xor gate inputs)
 - Gets confusing for large #s of ports
- Can specify the connecting ports by name
 - Helps avoid “misconnections”
 - Don’t have to remember port order
 - Can be easier to read
 - .<port name>(<signal name>)



35

Connections Examples

- Variables – defined in upper level module
 - wire [3:2] X; wire W_n; wire [3:0] word;
- By position
 - **module** dec_2_4_en (A, E_n, D);
 - dec_2_4_en DX (X[3:2], W_n, word);
- By name
 - **module** dec_2_4_en (A, E_n, D);
 - dec_2_4_en DX (.E_n(W_n), .A(X[3:2]), .D(word));
- In both cases,
A = X[3:2], E_n = W_n, D = word



36

Empty Port Connections

- Example: module dec_2_4_en(A, E_n, D);
 - dec_2_4_en DX (X[3:2], , word); // E_n is high impedance (z)
 - dec_2_4_en DX (X[3:2], W_n ,); // Outputs D[3:0] unused.
- General rules
 - Empty input ports => high impedance state (z)
 - Empty output ports => output not used
- Specify all input ports anyway!
 - Usually don't want z as input
 - Clearer to understand & find problems
- Helps if no connection to name port, but leave empty:
 - dec_2_4_en DX(.A(X[3:2]), .E_n(W_n), .D());

