

Digital Systems - Homework 06 - Group 5


Group members

No.	Name	ID
1	Vo Dong Ho	1752219
2	Nguyen Minh Nhat	1752039
3	Huynh Gia An Tien	1752538
4	Pham Minh Tuan	1752595
5	Thang Phu Vinh	1752624
6	Kang Minwoo	1652001
7	Nguyen Vu Thanh Nguyen	1652437
8	Tran Minh Hung	1652271

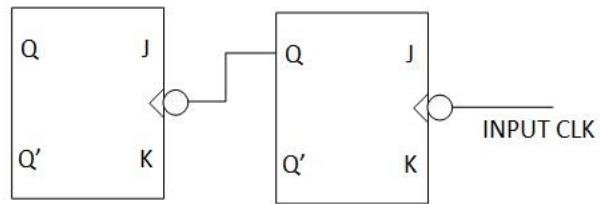
Problem 1. Ripple MOD4 Counter

- JK FF

Note: All J and K inputs are connected to 1.




- D FF

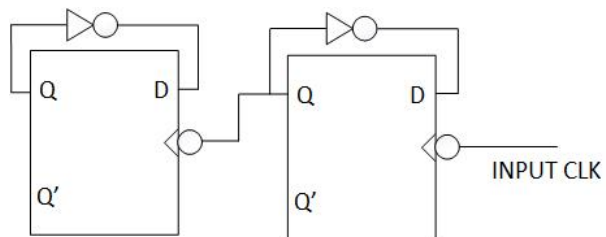

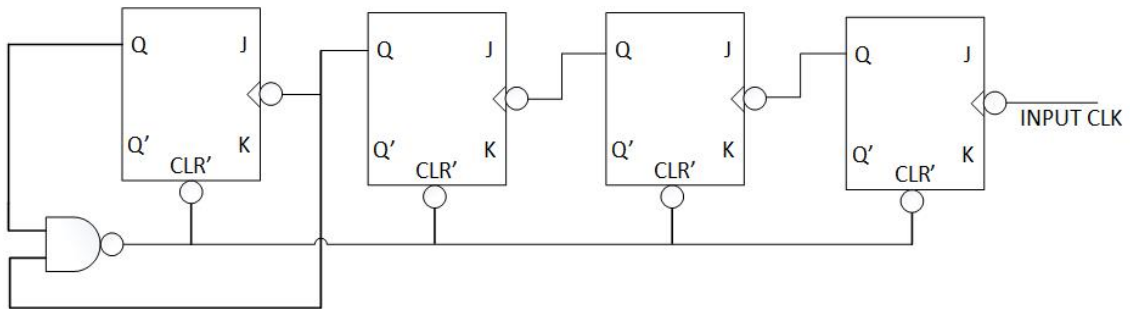
Problem 2. Ripple MOD12 Counter

- JK FF

Note: All J and K inputs are connected to 1.




- D FF

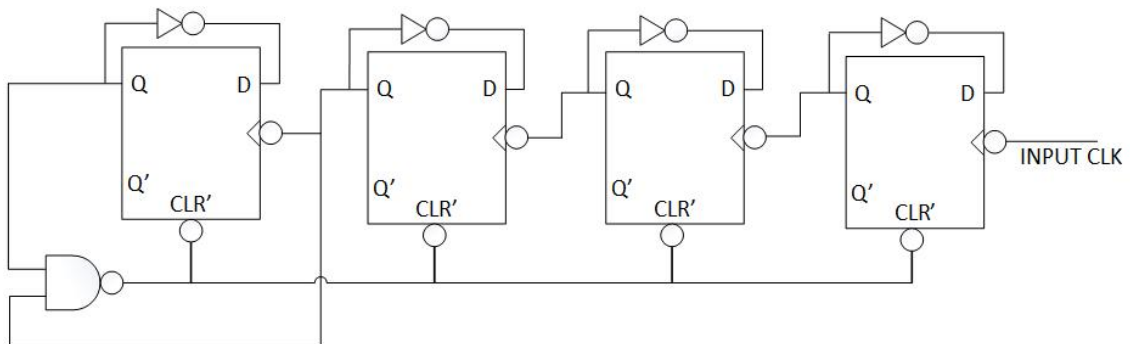

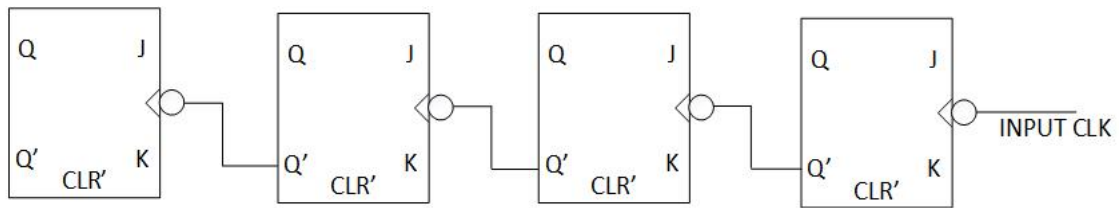
Problem 3. Ripple MOD16 Counter

- JK FF

Note: All J and K inputs are connected to 1.



- D FF

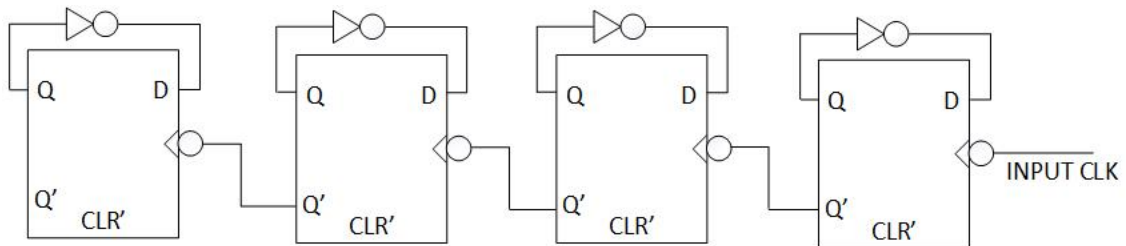


- Suppose the counter is in state 0110, determines the state of the counter after the next 27 clock cycles.

$$\begin{aligned} & (0110_2 + 27_{10})|16 \\ &= (6_{10} + 27_{10})|16 \\ &= 33|16 \\ &= 1_{10} = 0001_2 \end{aligned}$$

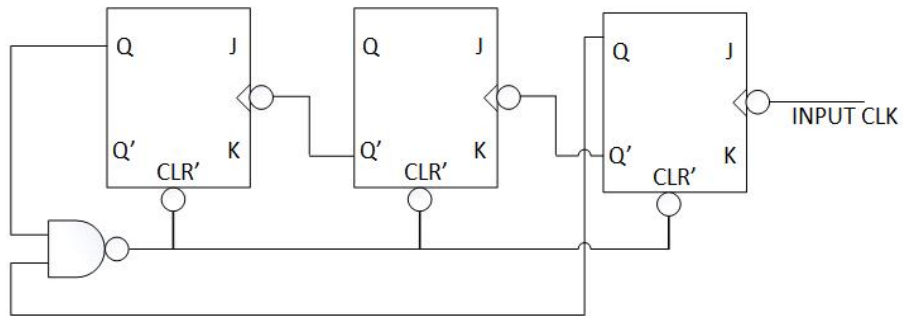
Problem 4. Ripple MOD5 Counter

- JK FF

Note: All J and K inputs are connected to 1.




- D FF

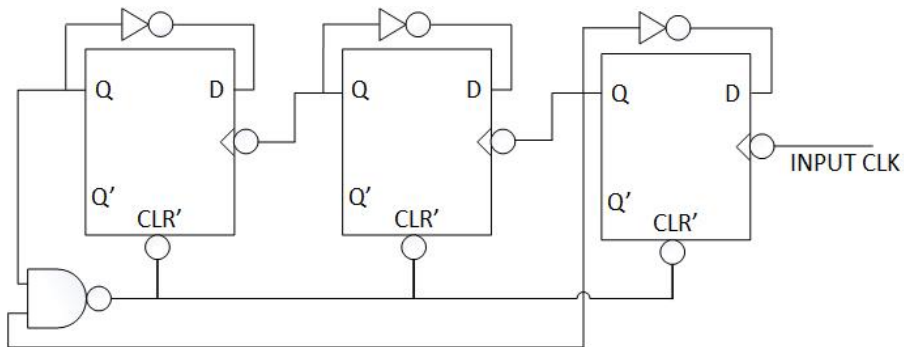

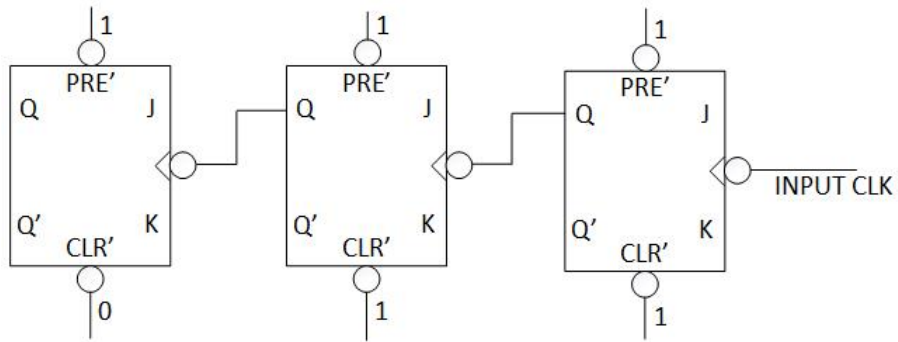
Problem 5. Asynchronous counter with sequence: $4 \rightarrow 5 \rightarrow 6 \rightarrow 7 \rightarrow 4$.

- **JK FF**

Note: All J and K inputs are connected to 1.




- **D FF**

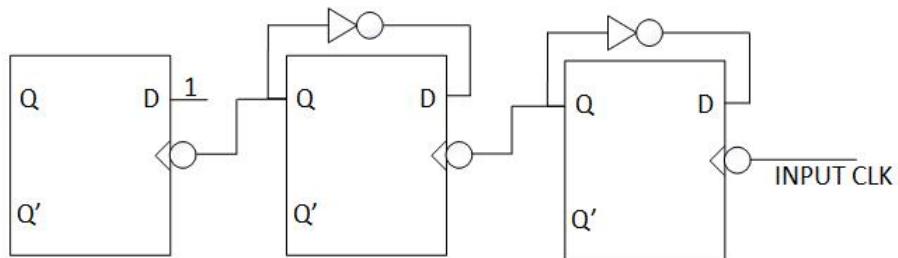

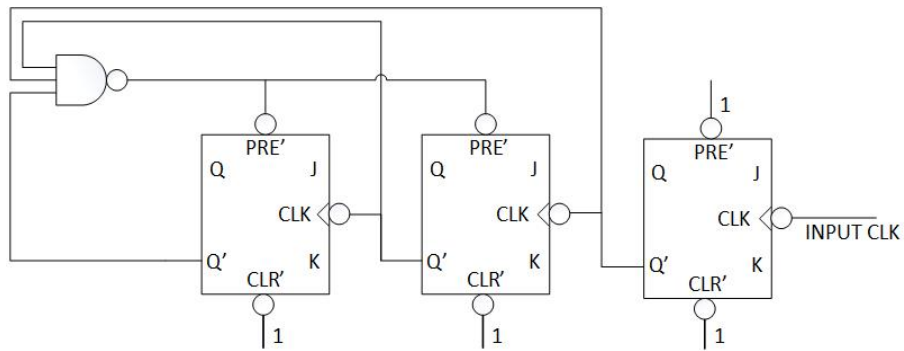
Problem 6. Asynchronous counter with sequence: $6 \rightarrow 5 \rightarrow 4 \rightarrow 3 \rightarrow 2 \rightarrow 1 \rightarrow 6$.

- JK FF

Note: All J and K inputs are connected to 1.



- D FF

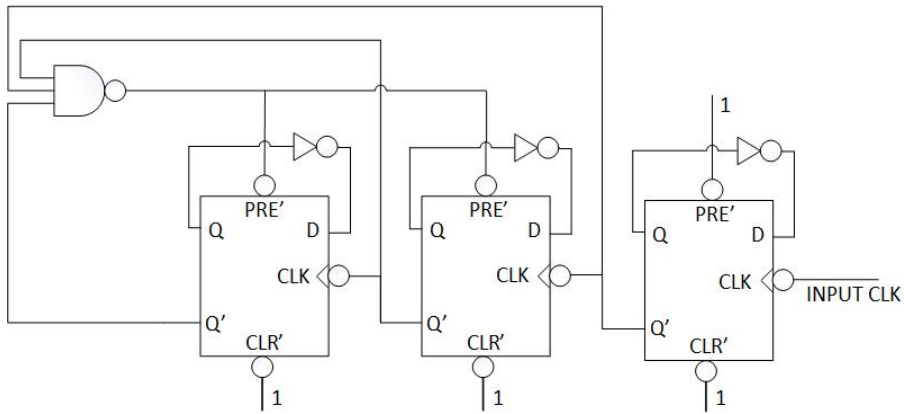

Problem 7.

(a) MOD of the counter:

- U_1 : MOD10
- U_2 : MOD7

\Rightarrow MOD of the counter: $10 \times 7 = 70$.

(b) Frequency of Q_3 of U_1 :

$$35000/2^4 = 2187.5(Hz)$$

(c) Frequency of Q_2 of U_2 :

$$35000/2^7 = 273.4375(Hz)$$

(d) Glitches:

- U_1 : Q_1, Q_3
- U_2 : Q_0, Q_1, Q_2

(e) Duty cycle of Q_2 of U_2 :

$$\frac{1}{35000/2^7} \times 50\% = 0.0018(s)$$

Problem 8.


(a) MOD of the counter: MOD12

(b) Glitches: C and D


(c) $f(B) = \frac{1}{2^2}f(CLK)$

(d) $f(D) = \frac{1}{2^4}f(CLK)$


Problem 9.

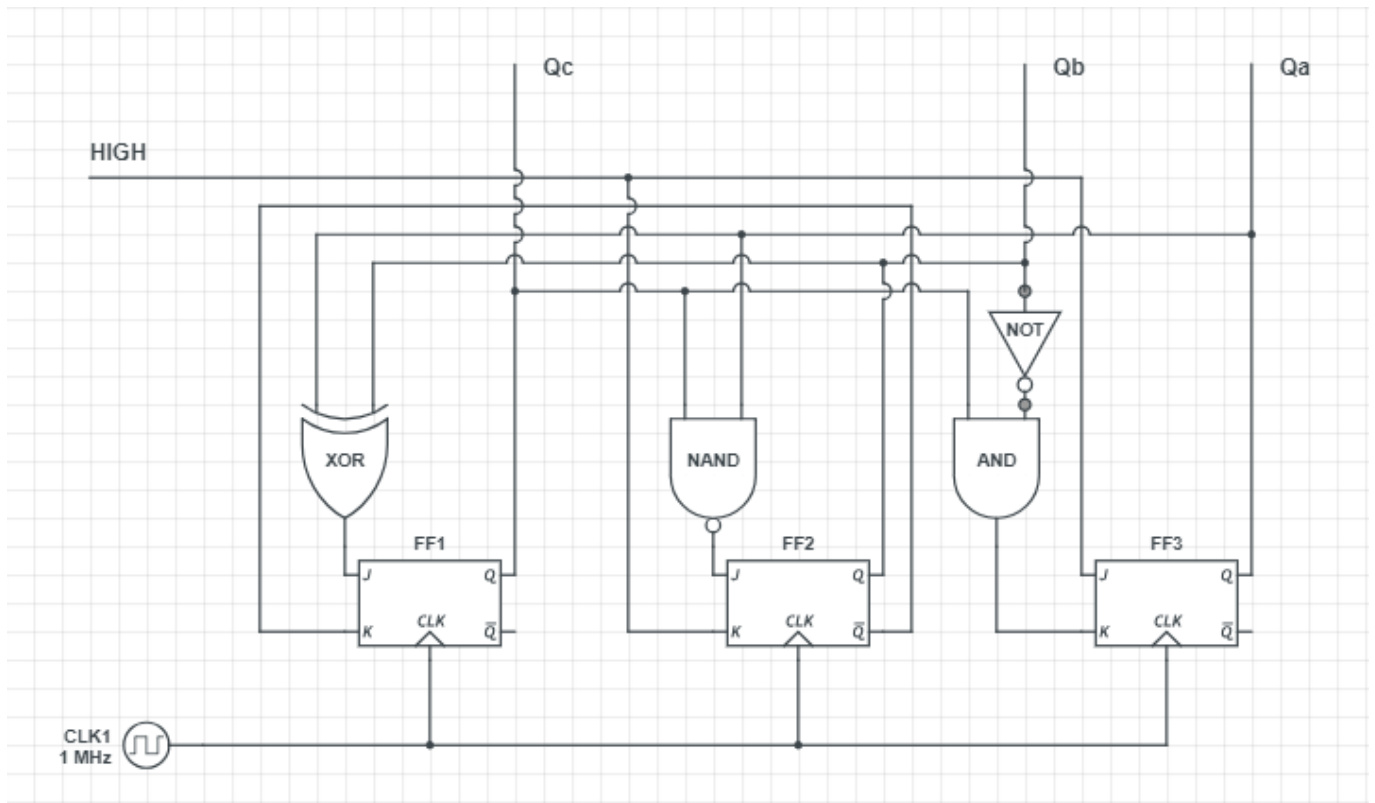

Problem 10.

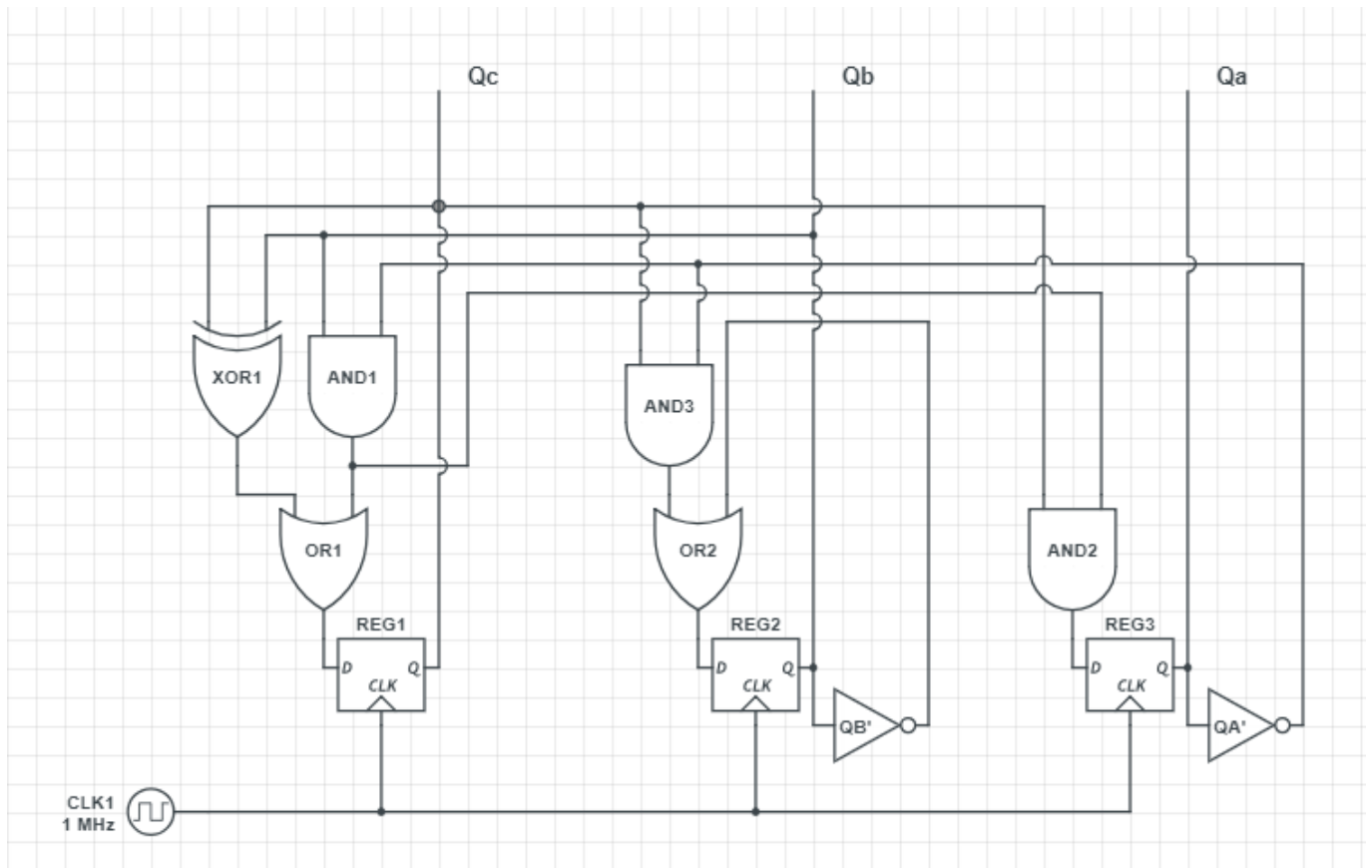

Problem 11.

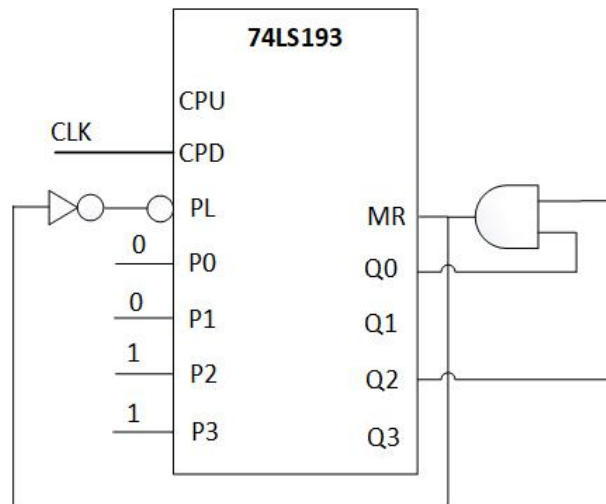

Problem 12.

$$000(\text{initial}) \rightarrow 100 \rightarrow 110 \rightarrow 111 \rightarrow 011 \rightarrow 001 \rightarrow 000(\text{initial})$$

Problem 13.

$$010(\text{initial}) \rightarrow 001 \rightarrow 000 \rightarrow 100 \rightarrow 011 \rightarrow 010(\text{initial})$$

Problem 14.

$$010(\text{initial}) \rightarrow 011 \rightarrow 100 \rightarrow 101 \rightarrow 110 \rightarrow 111 \rightarrow 000 \rightarrow 001 \rightarrow 010(\text{initial})$$